

The diagram on the left shows three circular icons arranged vertically. The bottom icon is a logic gate diagram. An arrow points from it to the middle icon, which is a purple square labeled 'CPU'. Another arrow points from the CPU icon to the top icon, which is a high-level logic diagram with various colored blocks and lines.

Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University
Modified slides by C. Wilcox, S. Rajopadhye Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Computing Layers

The diagram on the left is identical to the one in the first slide, showing the progression from a logic gate to a CPU to a high-level logic diagram.

- Problems
-
- Algorithms
-
- Language
-
- Instruction Set Architecture
-
- Microarchitecture
-
- Circuits ←
-
- Devices

CS270 - Fall 2013 - Colorado State University 2

Combinational vs. Sequential

● Combinational Circuit


- does not store information, always gives the same output for a given set of inputs
 - *example*: adder always generates sum and carry, regardless of previous inputs

● Sequential Circuit

- stores information, output depends on stored info (state) plus input
- so a given input might produce different outputs, depending on the stored information
- useful for building “memory” elements and “state machines”
 - *example*: ticket counter

R-S Latch: Simple Storage Element

 
- R is used to “reset” or “clear” the element – set it to zero.
- S is used to “set” the element – set it to one.




- If both R and S are one, output could be either zero or one.
 - “quiescent” state -- holds its previous value
 - if a is 1, b is 0, and vice versa

Clearing the R-S latch

 - Suppose we start with output = 1, then change R to zero.




Output changes to zero.

 


Then set R=1 to "store" value in quiescent state.

Setting the R-S Latch

 - Suppose we start with output = 0, then change S to zero.



Output changes to one.

 


Then set S=1 to "store" value in quiescent state.

R-S Latch Summary

- **R = S = 1**
 - hold current value in latch
- **S = 0, R=1**
 - set value to 1
- **R = 0, S = 1**
 - set value to 0
- **R = S = 0**
 - both outputs equal one
 - final state determined by electrical properties of gates
 - **Don't do it!**


Gated D-Latch

 - Two inputs: D (data) and WE (write enable)
 - when **WE = 1**, latch is set to **value of D**
 - **S = NOT(D), R = D**
 - when **WE = 0**, latch holds **previous value**
 - **S = R = 1**



Register

 - A register stores a multi-bit value.
 - We use a collection of D-latches, all controlled by a common WE.



Representing Multi-bit Values

- Number bits from right (0) to left (n-1)
 - just a convention -- could be left to right, but must be consistent

- Use brackets to denote range:
 $D[l:r]$ denotes bit l to bit r , from *left to right*

$$A = \overset{15}{0}1010011010101\overset{0}{1}$$

$$A[14:9] = 101001$$

$$A[2:0] = 101$$


- May also see $A\langle 14:9 \rangle$, especially in hardware block diagrams.

Memory

- Now that we know how to store bits, we can build a memory – a logical $k \times m$ array of stored bits.


Address Space:
number of locations
(usually a power of 2)

$k = 2^n$
locations

 

Addressability:
number of bits per location
(e.g., byte-addressable)

$2^2 \times 3$ Memory

 

More Memory Details

- Not the way actual memory is implemented!
 - fewer transistors, denser, relies on electrical properties
- But the logical structure is very similar.
 - address decoder, word select line, word write enable
- Random Access Memory: 2 different types
 - **Static RAM** (SRAM)
 - fast, used for caches, maintains data when powered
 - **Dynamic RAM** (DRAM)
 - slower but denser, storage decays, must be refreshed
- Non-Volatile Memory: **ROM, PROM, Flash**




Memory Bandwidth

- Bandwidth is the rate at which memory can be read or written by the processor.
- Approximately equal to the memory bus size times the speed at which the memory is clocked.
- Examples of bandwidth (from Wikipedia):
 - Phone line, Modem, up to 5.6KB/s
 - Digital subscriber line, ADSL, up to 128KB/s
 - Wireless networking, 802.11g, up to 17.5MB/s
 - Peripheral connection, USB 2.0, 60MB/s
 - Digital video, HDMI, up to 1.275GB/s
 - Computer bus, PCI Express, up to 25.6GB/s
 - Memory chips, SDRAM, up to 52GB/s

State Machine

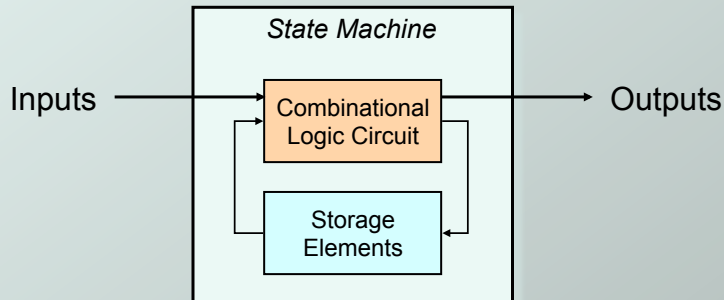- Another type of sequential circuit
 - Combines combinational logic with storage
 - “Remembers” state, and changes output (and state) based on **inputs** and **current state**



Combinational vs. Sequential

- Two types of “combination” locks



Combinational

Success depends only on the **values**, not the order in which they are set.

Sequential

Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).

State

- The **state** of a system is a **snapshot** of **all the relevant elements** of the system at the moment the snapshot is taken.

Examples:

- The state of a basketball game can be represented by the scoreboard: number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board.


State of Sequential Lock

Our lock example has four different states, labelled A-D:

- A: The lock is **not open**, and no relevant operations have been performed.
- B: The lock is **not open**, and the user has completed the **R-13** operation.
- C: The lock is **not open**, and the user has completed **R-13**, followed by **L-22**.
- D: The lock is **open**.

State Diagram

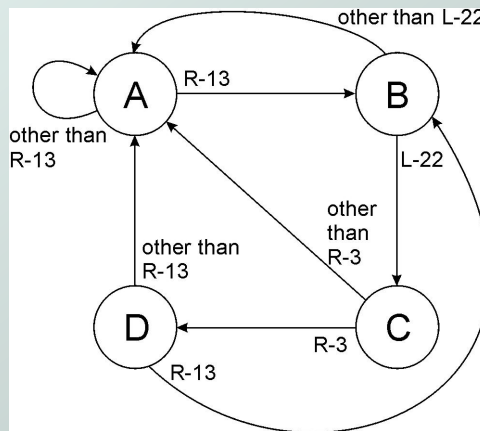- Shows **states** and **actions** that cause a **transition** between states.




Finite State Machine

- A system with the following components:
 1. A finite number of **states**
 2. A finite number of external **inputs**
 3. A finite number of external **outputs**
 4. An explicit specification of all **state transitions**
 5. An explicit specification of what determines each external **output value**
- Often described by a state diagram.
 - Inputs trigger state transitions.
 - Outputs are associated with each state (or with each transition).

The Clock

 
- Frequently, a **clock circuit** triggers transition from one state to the next.



- At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.
 - **Not always required.** In lock example, the input itself triggers a transition.


Implementing a Finite State Machine

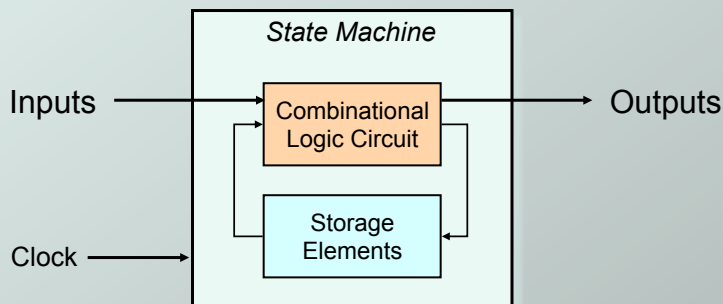- **Combinational logic**
 - Determine outputs and next state.
- **Storage elements**
 - Maintain state representation.



Storage: Master-Slave Flipflop

 - A pair of gated D-latches, to isolate *next* state from *current* state.



During 1st phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.


During 2nd phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.

Storage


- Each master-slave flipflop stores one state bit.
- The number of storage elements (flipflops) needed is determined by the number of states (and the representation of each state).
- Examples:
 - Sequential lock
 - Four states – two bits
 - Basketball scoreboard
 - 7 bits for each score, 5 bits for minutes, 6 bits for seconds, 1 bit for possession arrow, 1 bit for half, ...

Complete Example

 - A blinking traffic sign
 - No lights on
 - 1 & 2 on
 - 1, 2, 3, & 4 on
 - 1, 2, 3, 4, & 5 on
 - (repeat as long as switch is turned on)



Traffic Sign State Diagram

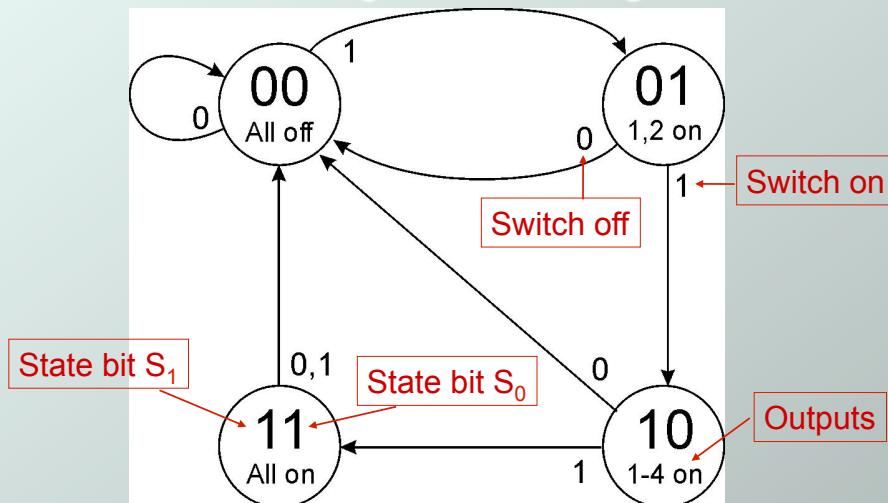

Transition on each clock cycle.

Traffic Sign Truth Tables

Outputs
(depend only on state: S_1S_0)

S_1	S_0	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1

Lights 1 and 2 → Z
Lights 3 and 4 → Y
Light 5 → X

Next State: S_1', S_0'
(depend on state and input)

In	S_1	S_0	S_1', S_0'
0	X	X	0 0
1	0	0	0 1
1	0	1	1 0
1	1	0	1 1
1	1	1	0 0

Whenever In=0, next state is 00.

Traffic Sign Logic

