

## Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University  
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Computing Layers

- Problems
- Algorithms
- Language
- Instruction Set Architecture
- Microarchitecture
- Circuits
- Devices ←

CS270 - Fall Semester 2016 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Transistor: Digital Building Blocks

- Microprocessors contain lots of transistors
  - Intel 8086 (1978): 29 thousand
  - Intel 80186 (1982): 55 thousand
  - Intel 80386 (1985): 275 thousand
  - Intel 80486 (1989): 1.1 million
  - Intel Pentium (1993): 3.1 million
  - Intel Pentium II (1998): 7.5 million
  - Intel Pentium III (2001): 45 million
  - Intel Pentium 4 (2006): 184 million
  - Intel Core 2 Duo (2006): 291 million
  - Intel Quad Core i7 (2011): 1.1 billion
  - Intel 8-core Xeon (2012): 2.3 billion

CS270 - Fall Semester 2016 3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


### Microprocessor Transistor Counts 1971-2011 & Moore's Law

CS270 - Fall Semester 2016 4

## Transistor: Digital Building Blocks

- Logically, each transistor acts as a switch
- Combined to implement logic functions (gates)
  - AND, OR, NOT
- Combined to build higher-level structures
  - Multiplexer, decoder, register, memory ...
  - Adder, multiplier ...
- Combined to build simple processor
  - LC-3

## Simple Switch Circuit

 

- Switch **open**:
  - Open circuit, no current
  - Light is **off**
  - $V_{out}$  is **+2.9V**
- Switch **closed**:
  - Short circuit across switch, current flows
  - Light is **on**
  - $V_{out}$  is **0V**




Switch-based circuits can easily represent two states: on/off, open/closed, voltage/no voltage.

## n-type MOS Transistor

- MOS = Metal Oxide Semiconductor
  - two types: n-type and p-type
   
### n-type

- when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
- when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)






Terminal #2 must be connected to GND (0V).
   
## p-type MOS Transistor


- p-type is *complementary* to n-type

- when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
- when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)




Terminal #1 must be connected to +2.9V.

## Physical Transistor

 


<http://en.wikipedia.org/wiki/CMOS>

## Transistor Output (Ideal)

 

Logic analyzer view of waveforms

## Transistor Output (Actual)

 

Actual waveform is not ideal!

## Propagation Delay

- Each gate has a propagation delay, typically fraction of a nanosecond ( $10^{-9}$  sec).
- Delays accumulate depending on the chain of gates the signals have to go through.
- Clock frequency of a processor is determined by the delay of the longest combinational path between storage elements, i.e. cycle time.

## Logic Gates

- Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.
- Digital symbols:
  - recall that we assign a range of analog voltages to each digital (logic) symbol





- assignment of voltage ranges depends on electrical properties of transistors being used
  - typical values for "1": +5V, +3.3V, +2.9V
  - from now on we'll use +2.9V

## CMOS Circuit

- Complementary MOS**
- Uses both **n-type** and **p-type** MOS transistors
  - p-type
    - Attached to + voltage
    - Pulls output voltage UP when input is zero
  - n-type
    - Attached to GND
    - Pulls output voltage DOWN when input is one
- For all inputs, make sure that output is either connected to GND or to +, but not both!**

## Inverter (NOT Gate)

  

In	Out	In	Out
0 V	2.9 V	0	1
2.9 V	0 V	1	0

Truth table

## Logical Operation: OR and NOR

A	B	OR
0	0	0
0	1	1
1	0	1
1	1	1

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Inputs: 2 or more



Output=A+B



Output= $\overline{A+B}$

## AND and NAND

A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0





Output =  $A \cdot B$

Inputs: 2 or more



Output =  $\overline{A \cdot B}$

## NOR Gate (Not of OR)

  


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Truth table

Note: Serial structure on top, parallel on bottom.

## OR Gate


 


A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Truth table

Add inverter to NOR.

## NAND Gate (AND-NOT)

  

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

Note: Parallel structure on top, serial on bottom.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## AND Gate

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

**Truth table**

Add inverter to NAND.

CS270 - Fall Semester 2016 21

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Basic Logic Gates

A — NOT —  $\bar{A}$

**NOT**

A B — OR —  $A+B$

**OR**

A B — NOR —  $\overline{A+B}$

**NOR**

A B — AND —  $AB$

**AND**

A B — NAND —  $\overline{AB}$

**NAND**

CS270 - Fall Semester 2016 22

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Boolean Algebra

$x \cdot 0 = 0$

$x \cdot 1 = x$

$x \cdot \bar{x} = 0$

$x + 0 = x$

$x + 1 = 1$

$x + \bar{x} = 1$

Remember Identify, Domination, Negation Laws from Logic!

CS270 - Fall Semester 2016

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

## Boolean Algebra Laws

- **Commutative**
  - $A+B = B+A$
  - $A \cdot B = B \cdot A$
- **Associative**
  - $A+(B+C)=(A+B)+C = \mathbf{A+B+C}$
  - $A \cdot (B \cdot C)=(A \cdot B) \cdot C = \mathbf{ABC}$
- **Distributive**
  - $A \cdot (B+C)=A \cdot B+A \cdot C$
  - $A+(B \cdot C)=(A+B) \cdot (A+C)$

CS270 - Fall Semester 2016

## Useful Simplification Identities

◆  $\overline{AB} + AB = A$


Proof:  $\overline{AB} + AB = \overline{A(B+B)}$  // **Distributive Law**  
 $= A(T)$  // **Negation Law**  
 $= A$  // **Identity Law**

◆  $A + AB = A$

Proof:  $A + AB = A(1+B)$  // **Distributive Law**  
 $= A(1)$  // **Domination Law**  
 $= A$  // **Identity Law**
 
## DeMorgan's Law

- ◆ Converting AND to OR (with some help from NOT)
- ◆ Consider the following gate:




A	B	$\overline{A}$	$\overline{B}$	$\overline{A \cdot B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

To convert AND to OR  
(or vice versa),  
invert inputs and output.

Same as A OR B!
 
## More than 2 Inputs?

- ◆ AND/OR can take any number of inputs.
  - AND = 1 if all inputs are 1.
  - OR = 1 if any input is 1.
  - Similar for NAND/NOR.
- ◆ Can implement with multiple two-input gates, or with single CMOS circuit.



## Summary

- ◆ MOS transistors are used as switches to implement logic functions.
  - n-type: connect to GND, turn on (1) to pull down to 0
  - p-type: connect to +2.9V, turn on (0) to pull up to 1
- ◆ Basic gates: NOT, NOR, NAND
  - Logic functions are usually expressed with AND, OR, and NOT
- ◆ DeMorgan's Law
  - Convert AND to OR (and vice versa) by inverting inputs and output



## Building Functions from Logic Gates

- **Combinational Logic Circuit**
  - output depends only on the current inputs
  - stateless
- **Sequential Logic Circuit**
  - output depends on the sequence of inputs (past and present)
  - stores information (state) from past inputs
- We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.

## Building Complex Functions

Start with a truth table. Two approaches

- **Use gates as the building block**
  - Systematically derive the circuit
    - one row = one gate
    - minimize the gates (e.g., K-maps, QMCC)
- **Use transistors directly as building blocks**
  - Translate the truth table into a circuit for the **pull-up** circuit
  - Also translate it into a different circuit for the **pull-down** circuit
  - Both are very closely related – so **transform** the pull-up circuit into the pull-down circuit

## Series Parallel Circuits (SPC)

- Simple (recursive) rules to define an important family of circuits
- Useful to design combinational logic
- Expose/reinforce recursive thinking
- Alternative view of basic concepts
  - Universality
  - Transformations & Equivalence

## SPC Recursive Rules

- A single transistor by itself is a series-parallel circuit (with source and drain defining the "direction" of current flow, i.e., **input** and **output**)
- **SPCs in series make an SPC.** If X and Y are SPC's
  - Connect the output of X to input of Y
  - Input of X is the input of the new circuit
  - Output of Y is the output of the new SPC
- **SPCs in parallel make an SPC.** If X and Y are SPC's
  - Connect inputs of X and Y, and outputs of X and Y
  - Input of X (or Y) is the input of the new circuit
  - Output of X (or Y) is the output of the new SPC



## Two more rules

- ◆ Nothing else is an SPC (the previous rules are “complete”)
- ◆ All transistors in an SPC must be of the same type
  - either all p-type
  - or all n-type
  - this is the **type** of the SPC

## SPCs to design Boolean functions

Describe the desired circuit behavior as a truth table, and design p-type SPC as the “pull up” and an n-type SPC as the “pull down”

- ◆ For every input combination where the output is 1
  - The **pull up circuit** must provide a path between  $V_{DD}$  and the output
- ◆ For every input combination where the output is 0
  - The **pull down circuit** must provide a path between GND and the output

## Pull-up Circuit

- ◆ One (**parallel**) branch for each row where the output is 1: each row is an “or-alternative” so branches are in parallel
- ◆ Each such branch has one transistor in **series** for each term in the row  
Each term must have the specified value (AND = **series**)
  - If term is zero, the gate is the input signal
  - If term is 1, gate is the negation of input
- ◆ Example on doc-cam

## Pull-down Circuit

- ◆ For every truth table row with a 0 output
  - Provide a path from the output to GND
  - Connect all the paths in parallel
- ◆ Either design it from scratch like the pull-up circuit
- ◆ Or equivalently, simply construct the **complement** of the pull-up circuit
- ◆ Follows from DeMorgan’s Laws

## Recursive Rules for Complement

- The complement of n SPC with a single transistor is the complement of the transistor
- If an SPC is the **series composition** of two (or more) SPC's, X and Y
  - Its complement is the **parallel connection** of the individual complements of X and Y
- If SPC is the parallel composition of two (or more) SPC's, X and Y
  - Its complement is the **serial connection** of the individual complements of X and Y