

Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Computing Layers

Problems

Algorithms

Language

Instruction Set Architecture

Microarchitecture

Circuits ←

Devices

CS270 - Fall Semester 2016 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Combinational vs. Sequential

- **Combinational Circuit**
 - does not store information, always gives the same output for a given set of inputs
 - *example*: adder always generates sum and carry, regardless of previous inputs
- **Sequential Circuit**
 - stores information, output depends on stored info (state) plus input
 - so a given input might produce different outputs, depending on the stored information
 - useful for building “memory” elements and “state machines”
 - *example*: ticket counter

CS270 - Fall Semester 2016 3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

R-S Latch: Simple Storage Element


- R is used to “reset” or “clear” the element – set it to zero.
- S is used to “set” the element – set it to one.

- If both R and S are one, output could be either zero or one.
 - “quiescent” state -- holds its previous value
 - if a is 1, b is 0, and vice versa


CS270 - Fall Semester 2016 4

Clearing the R-S latch

 - Suppose we start with output = 1, then change R to zero.




Output changes to zero.

 


Then set R=1 to "store" value in quiescent state.

Setting the R-S Latch

 - Suppose we start with output = 0, then change S to zero.



Output changes to one.

 


Then set S=1 to "store" value in quiescent state.

R-S Latch Summary

- R = S = 1**
 - hold current value in latch
- S = 0, R=1**
 - set value to 1
- R = 0, S = 1**
 - set value to 0
- R = S = 0**
 - both outputs equal one
 - final state determined by electrical properties of gates if you transition to R = S = 1.
 - Don't do it!**


Gated D-Latch

 - Two inputs: D (data) and WE (write enable)
 - when **WE = 1**, latch is set to **value of D**
 - S = NOT(D), R = D
 - when **WE = 0**, latch holds **previous value**
 - S = R = 1



Register

 - A register stores a multi-bit value.
 - We use a collection of D-latches, all controlled by a common WE.




Memory

- Now that we know how to store bits, we can build a memory – a logical $k \times m$ array of stored bits.


Address Space:
number of locations
(usually a power of 2)

$k = 2^n$
locations

 Addressability:
number of bits per location
(e.g., byte-addressable)




$2^2 \times 3$ Memory

 

More Memory Details

- Not the way actual memory is implemented!
 - fewer transistors, denser, relies on electrical properties
- But the logical structure is very similar.
 - address decoder, word select line, word write enable
- Random Access Memory: 2 different types
 - **Static RAM (SRAM)**
 - fast, used for caches, maintains data when powered
 - **Dynamic RAM (DRAM)**
 - slower but denser, storage decays, must be refreshed
- Non-Volatile Memory: **ROM, PROM, Flash**

 

Memory Bandwidth

- Bandwidth is the rate at which memory can be read or written by the processor.
- Approximately equal to the memory bus size times the speed at which the memory is clocked.
- Examples of bandwidth (from Wikipedia):
 - Phone line, Modem, up to 5.6KB/s
 - Digital subscriber line, ADSL, up to 128KB/s
 - Wireless networking, 802.11g, up to 17.5MB/s
 - Peripheral connection, USB 2.0, 60MB/s
 - Digital video, HDMI, up to 1.275GB/s
 - Computer bus, PCI Express, up to 25.6GB/s
 - Memory chips, SDRAM, up to 52GB/s