

Chapter 3 Digital Logic Structures

Original slides from Gregory Byrd, North Carolina State University
Modified slides by Chris Wilcox, Colorado State University

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Computing Layers

- Problems
-
- Algorithms
-
- Language
-
- Instruction Set Architecture
-
- Microarchitecture
-
- Circuits ←
-
- Devices

CS270 - Fall Semester 2016 2

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

State Machine

- Another type of sequential circuit
 - Combines combinational logic with storage
 - “Remembers” state, and changes output (and state) based on **inputs** and **current state**

CS270 - Fall Semester 2016 3

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Combinational vs. Sequential

- Two types of “combination” locks

Combinational
Success depends only on the **values**, not the order in which they are set.

Sequential
Success depends on the **sequence** of values (e.g., R-13, L-22, R-3).

CS270 - Fall Semester 2016 4

State

- The **state** of a system is a **snapshot** of **all the relevant elements** of the system at the moment the snapshot is taken.

Examples:

- The state of a basketball game can be represented by the scoreboard: number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board.


State of Sequential Lock

Our lock example has four different states, labelled A-D:

- A: The lock is **not open**, and no relevant operations have been performed.
- B: The lock is **not open**, and the user has completed the **R-13** operation.
- C: The lock is **not open**, and the user has completed **R-13**, followed by **L-22**.
- D: The lock is **open**.

State Diagram

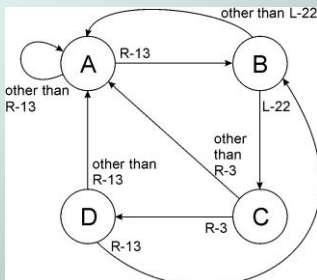- Shows **states** and **actions** that cause a **transition** between states.




Finite State Machine

- A system with the following components:
 1. A finite number of **states**
 2. A finite number of external **inputs**
 3. A finite number of external **outputs**
 4. An explicit specification of all **state transitions**
 5. An explicit specification of what determines each external **output value**
- Often described by a state diagram.
 - Inputs trigger state transitions.
 - Outputs are associated with each state (or with each transition).

The Clock

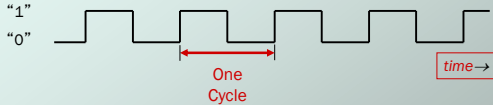
- Frequently, a **clock circuit** triggers transition from one state to the next.



- At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.
 - **Not always required.** In lock example, the input itself triggers a transition.


Implementing a Finite State Machine

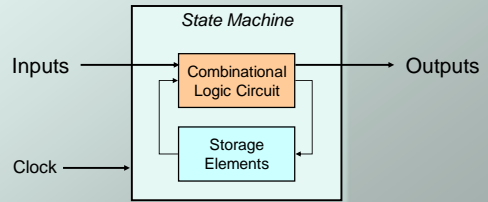- **Combinational logic**
 - Determine outputs and next state.
- **Storage elements**
 - Maintain state representation.



Storage: Master-Slave Flipflop

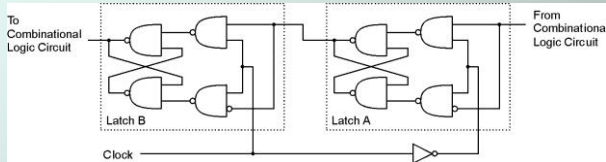- A pair of gated D-latches, to isolate *next* state from *current* state.



During 1st phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.


During 2nd phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.

Storage


- Each master-slave flipflop stores one state bit.
- The number of storage elements (flipflops) needed is determined by the number of states (and the representation of each state).
- Examples:
 - Sequential lock
 - Four states – two bits
 - Basketball scoreboard
 - 7 bits for each score, 5 bits for minutes, 6 bits for seconds, 1 bit for possession arrow, 1 bit for half, ...

Complete Example

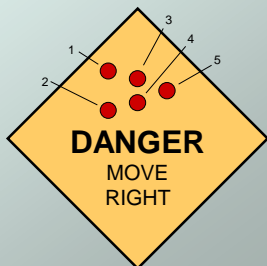- A blinking traffic sign
 - No lights on
 - 1 & 2 on
 - 1, 2, 3, & 4 on
 - 1, 2, 3, 4, & 5 on
 - (repeat as long as switch is turned on)



Traffic Sign State Diagram

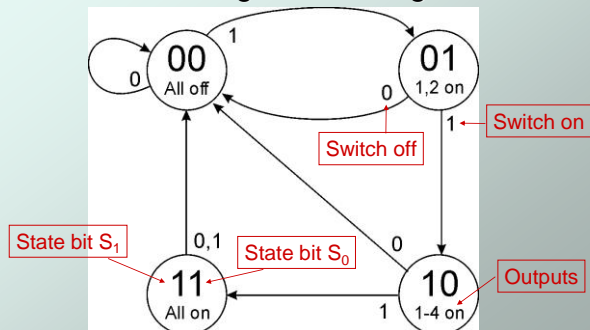

Transition on each clock cycle.

Traffic Sign Truth Tables


Outputs (depend only on state: $S_1 S_0$)

S_1	S_0	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1

Next State: $S_1' S_0'$ (depend on state and input)

In	S_1	S_0	S_1'	S_0'
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Traffic Sign Logic

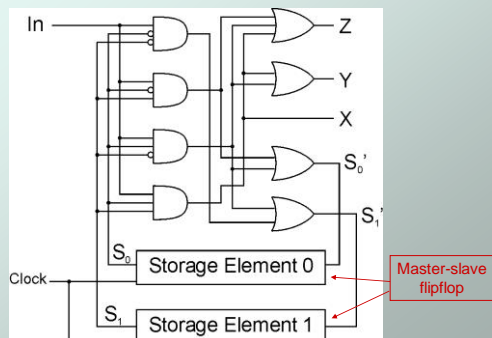

From Logic to Data Path

- The data path of a computer is all the logic used to process information.
 - See the data path of the LC-3 on next slide.
- **Combinational Logic**
 - Decoders -- convert instructions into control signals
 - Multiplexers -- select inputs and outputs
 - ALU (Arithmetic and Logic Unit) -- operations on data
- **Sequential Logic**
 - State machine -- coordinate control signals and data movement
 - Registers and latches -- storage elements

LC-3 Data Path

Combinational Logic

Storage

State Machine

