



# Lecture 22

## Chapters 3

### Logic Circuits Part 1



# Computing Layers

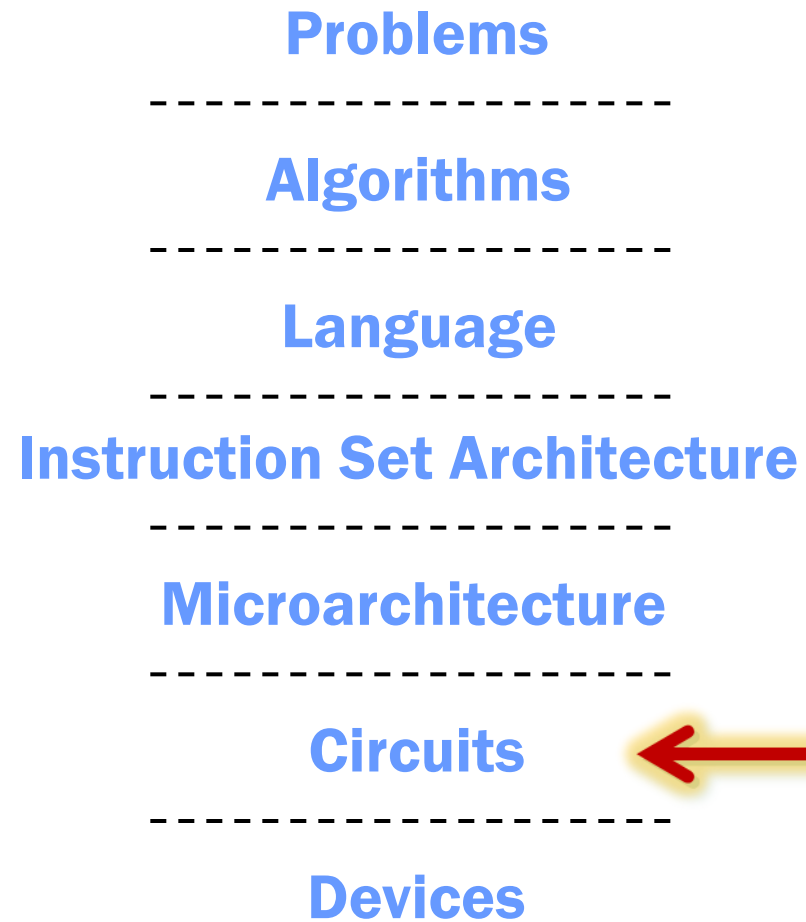 

# Transistor: Building Block of Computers

**Logically, each transistor acts as a switch**

**Combined to implement logic functions (gates)**

- AND, OR, NOT


**Combined to build higher-level structures**

- Adder, multiplexer, decoder, register, memory ...
- Adder, multiplier ...

**Combined to build simple processor**

- LC-3

# Simple Switch Circuit

 

## Switch **open**:

- Open circuit, no current
- Light is **off**
- $V_{out}$  is **+2.9V**

## Switch **closed**:

- Short circuit across switch, current flows
- Light is **on**
- $V_{out}$  is **0V**

*Switch-based circuits* can easily represent two states: on/off, open/closed, voltage/no voltage.

# n-type MOS Transistor


MOS = Metal Oxide Semiconductor

- two types: n-type and p-type
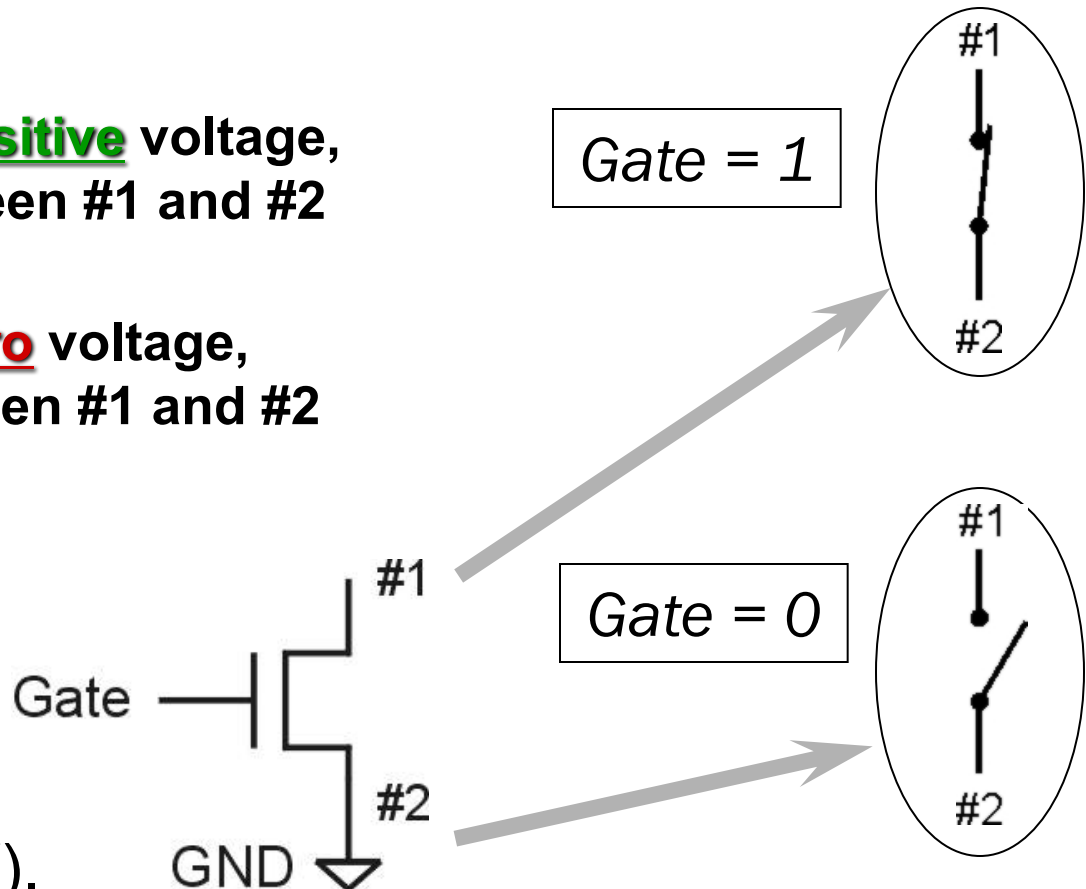
## n-type

- when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
- when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)


Terminal #2 must be connected to GND (0V).


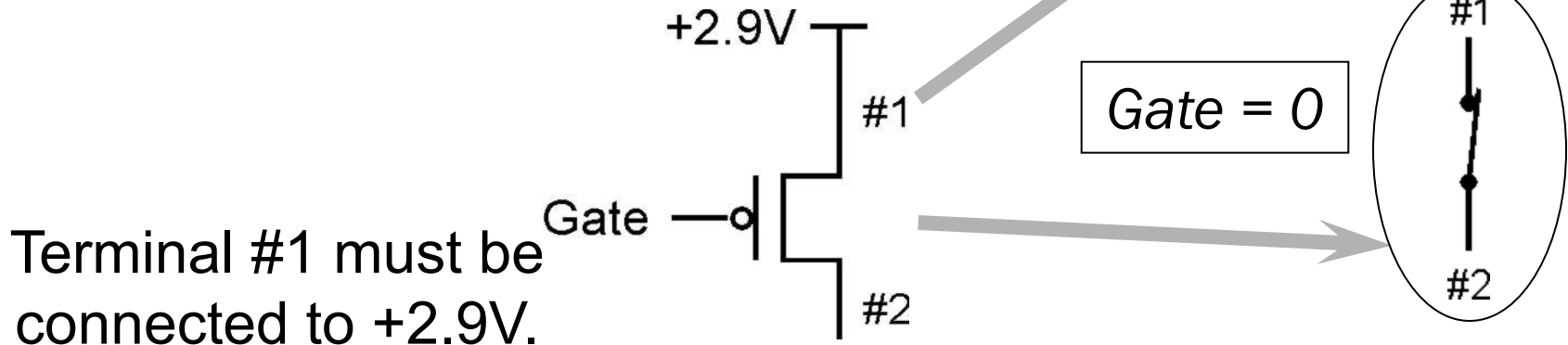
# p-type MOS Transistor

**p-type** is *complementary* to n-type

- when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
- when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)



# Logic Gates

Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.

Digital symbols:

- recall that we assign a range of analog voltages to each digital (logic) symbol



- assignment of voltage ranges depends on electrical properties of transistors being used
  - typical values for "1": +5V, +3.3V, +2.9V
  - from now on we'll use +2.9V



# CMOS Circuit



**Complementary** MOS uses both **n-type** and **p-type** MOS transistors

- p-type
  - Attached to + voltage (2.9v)
  - Pulls output voltage UP when input is zero
- n-type
  - Attached to GND (0v)
  - Pulls output voltage DOWN when input is one

For all inputs, output is either connected to GND or to +, but not both!

No direct connection between + and GND, except switching. **Low power consumption.**

# Inverter (NOT Gate)

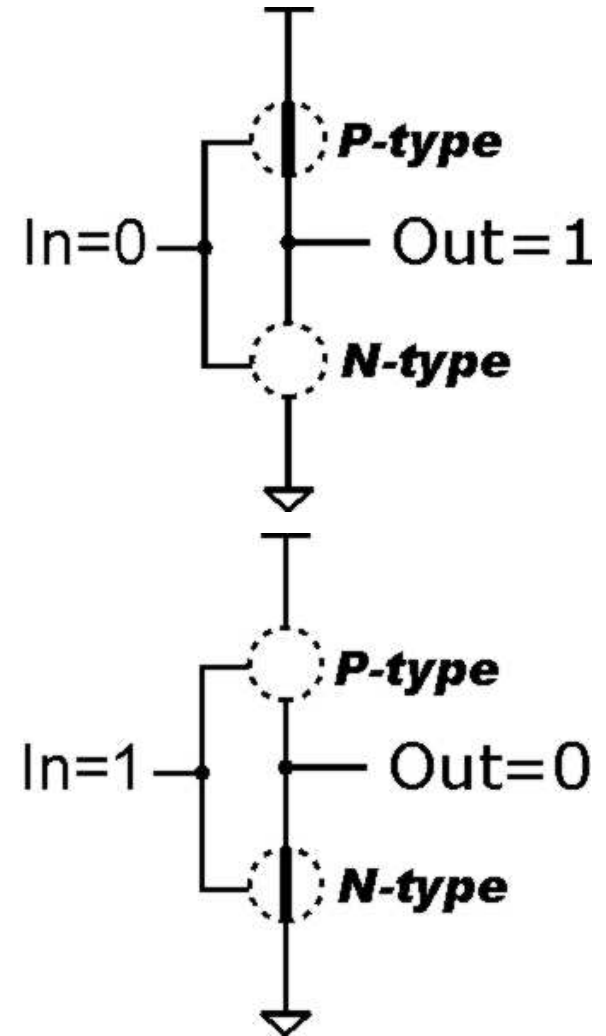 

In	Out	In	Out
0 V	2.9 V	0	1
2.9 V	0 V	1	0

*Truth table*


# Logical Operation: OR and NOR

Truth tables


A	B	OR
0	0	0
0	1	1
1	0	1
1	1	1

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Inputs: *2 or more*

 

Logic symbols

 

$$\text{Output} = A + B$$

Boolean algebra notation


$$\text{Output} = \overline{A + B}$$

# AND and NAND


A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

Inputs: 2 or more

 


Output =  $A.B$


 


Output =  $\overline{A.B}$

# NOR Gate (OR-NOT)

 

Logic symbol

  


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

**Truth table**

Note: Serial structure on top, parallel on bottom.

# OR Gate

 


A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


*Truth table*

*Add inverter to NOR.*


# Basic Logic Gates

 


*NOT*

 


*OR*

 

*NOR*

 


*AND*

 


*NAND*


# Boolean Algebra

 


$$X \cdot 0 = 0$$

 


$$X \cdot 1 = X$$

 


$$X \cdot \bar{X} = 0$$

 

$$X + 0 = X$$

 

$$X + 1 = 1$$

 

$$X + \bar{X} = 1$$



## Boolean Algebra Laws (2)

**Commutative**  $A+B = B+A$        $A.B = B.A$

**Associative**

- $A+(B+C)=(A+B)+C = A+B+C$
- $A.(B.C)=(A.B).C = ABC$

**Distributive**

- $A.(B+C)=A.B+A.C$
- $A+(B.C)=(A+B).(A+C)$

## Some Useful Identities for simplification

$$AB + A\bar{B} = A$$

$$\begin{aligned}\text{Proof: } AB + A\bar{B} &= A(B + \bar{B}) \\ &= A\end{aligned}$$


$$A + AB = A$$

$$\begin{aligned}\text{Proof: } A + AB &= A(1 + B) \\ &= A\end{aligned}$$

# DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:

 

A	B	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as A OR B!


*To convert AND to OR  
(or vice versa),  
invert inputs and output.*

## More than 2 Inputs?

**AND/OR can take any number of inputs.**

- **AND = 1 if all inputs are 1.**
- **OR = 1 if any input is 1.**
- **Similar for NAND/NOR.**

 **Can implement with multiple two-input gates, or with single CMOS circuit.**



## Propagation Delay

- Each gate has a propagation delay, typically fraction of a nanosecond ( $10^{-9}$  sec).
- Delays add depending on the chain of gates the signals have to go through.
- Clock frequency is determined by the delay of the longest combinational path between storage elements. Measured in GHz ( $10^9$  cycles per sec).

# Summary

**MOS transistors are used as switches to implement logic functions.**

- **n-type: connect to GND, turn on (1) to pull down to 0**
- **p-type: connect to +2.9V, turn on (0) to pull up to 1**

**Basic gates: NOT, NOR, NAND**

- **Boolean Algebra: Logic functions are usually expressed with AND, OR, and NOT**

**DeMorgan's Law**

- **Convert AND to OR (and vice versa) by inverting inputs and output**

# Building Functions from Logic Gates

## *Combinational Logic Circuit*

- output depends only on the current inputs
- stateless


## *Sequential Logic Circuit*

- output depends on the sequence of inputs (past and present)
- stores information (state) from past inputs

**We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.**

# Combinatorial Logic

## Cascading set of logic gates

 

Digital circuit

A	B	C	W	X	Y	Z
0	0	0	0	0	0	1
0	0	1	0	1	1	1
0	1	0	0	1	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	0	0

Truth table



# Logisim Simulator

- **Logic simulator: allows interactive design and layout of circuits with AND, OR, and NOT gates**
- **Simulator web page (linked on class web page)**  
<http://www.cburch.com/logisim>
- **Overview, tutorial, downloads, etc.**
- **Windows or Linux operating systems**
- **Logisim demonstration**

# Functional Blocks


- **Decoder**
- **Multiplexer**
- **Full Adder**
- **Any general function**

# Decoder

$n$  inputs,  $2^n$  outputs

- exactly one output is 1 for each possible input pattern


*2-bit  
decoder*

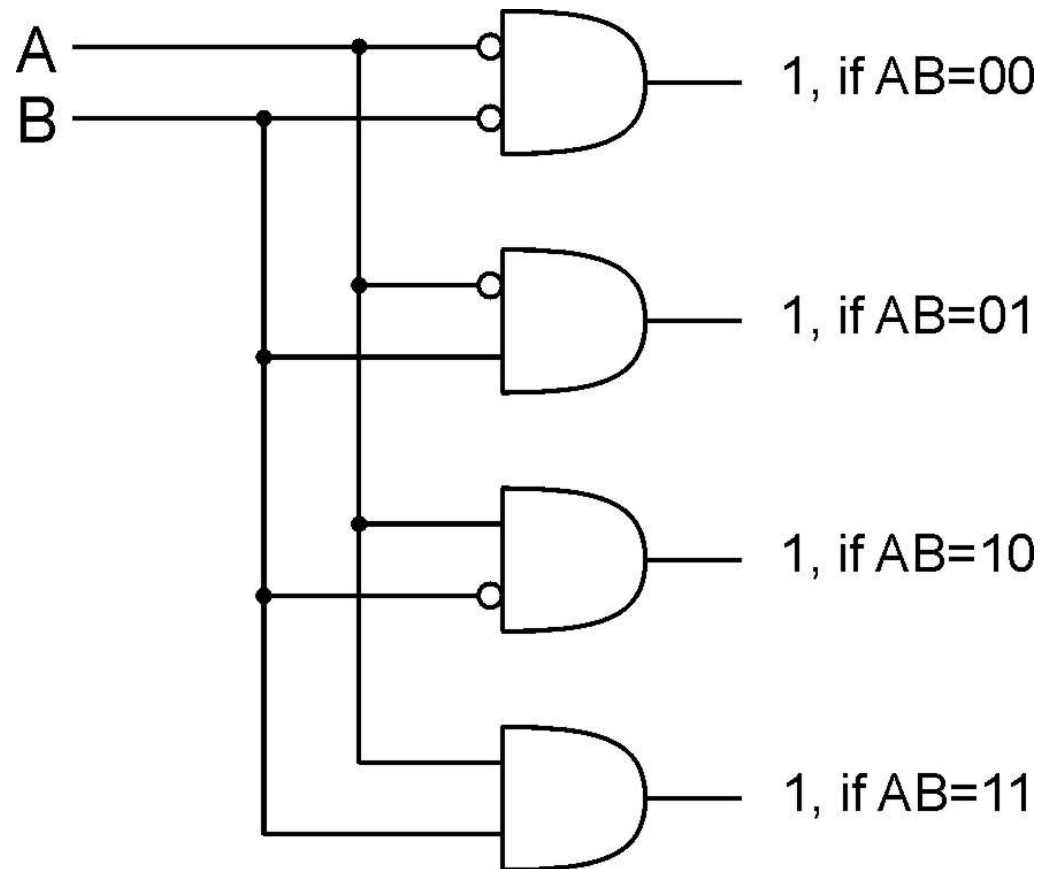

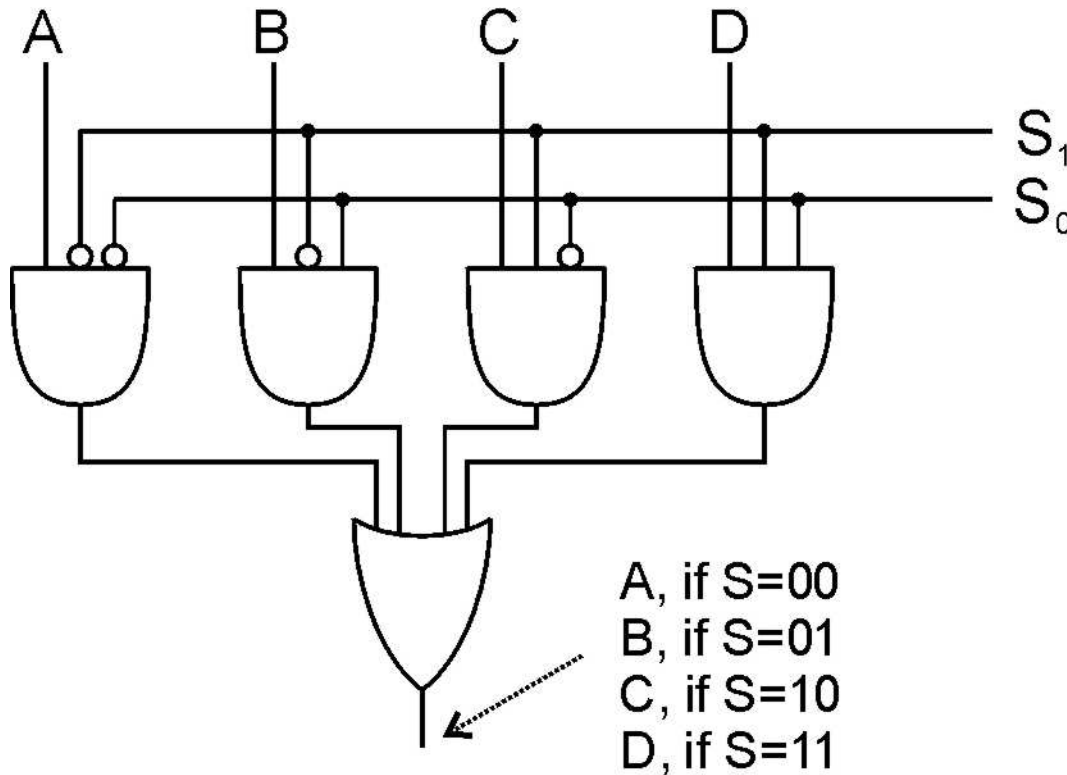
# Multiplexer (MUX)

$n$ -bit selector and  $2^n$  inputs, one output

- output equals one of the inputs, depending on selector




Functional representation

 

*4-to-1 MUX*

 
# Full Adder

Add two bits and carry-in,  
produce one-bit sum and carry-out.



A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Four-bit Adder (*ripple carry*)

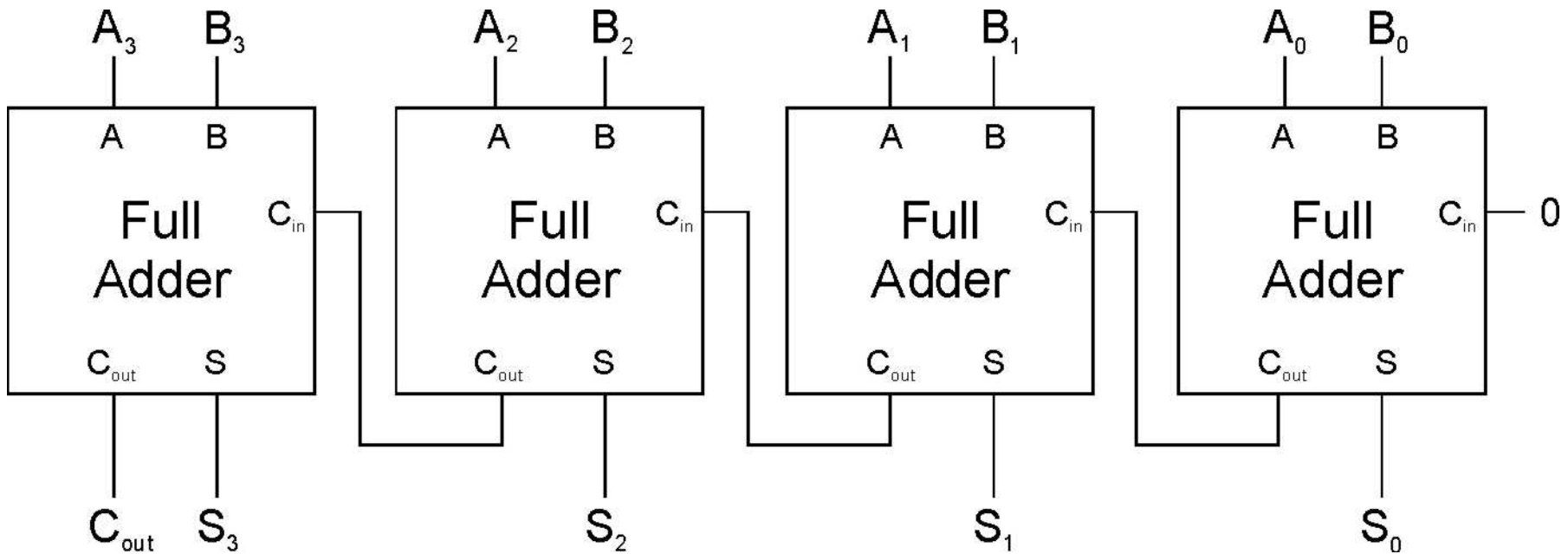


2 levels of delay per stage

# Logical Completeness

Can implement ANY truth table with combo of **AND**, **OR**, **NOT** gates.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

1. AND combinations that yield a "1" in the truth table.
2. OR the results of the AND gates.

## Truth Table (to circuit)

How do we design a circuit for this?

A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1




# Programmable Logic Array

**Front end is decoder for inputs**

**Back end defines the outputs**

**Any truth table can be built**

**Not necessarily minimal circuit!**

 


**Requires (at least) ten gates.**
 
# Circuit Minimization using Boolean Algebra

Boolean logic lets us reduce the circuit

- $X = A'B'C' + A'BC' + ABC' + ABC =$   
 $= A'C' + AB$
- $Y = A'B'C + A'BC + AB'C + ABC$   
 $= A'C + AC = C$



A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

Try with Logisim!

# Karnaugh maps to minimize literals

Based on set-theory

- Visual representation of algebraic functions
- Allow algorithmic minimization of boolean functions in sum-of-products form
- “adjacent” terms can be combined.
  - Adjacent: differ in one variable, complemented in one, not complemented in the other.

## Example:

- $ABC + ABC' = AB(C + C') = AB$
- Thus  $ABC$  and  $ABC'$  are two pieces of  $AB$ .

## Combining Minterms

- For  $n$ -variables, there are  $2^n$  minterms, corresponding to each row of truth table.
- Some of them can be combined into groups of 2, (or 4 or 8 ..) to simplify the function.

# Karnaugh maps

Visual representation of algebraic functions to make it easy to spot “adjacent” minterms”

- Columns arranged so that *adjacent terms* are visually adjacent.
- Identify groups of 2, 4, 8 etc. terms that can be combined.
- All 1's must be covered.
- A 1 can be used more than once, if needed.
- Sometimes the solution is not unique
- Next: maps for  $X(A,B,C)$  and  $Y(A,B,C)$

A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

# Karnaugh Maps: Visualization of algebra

A	B	C	X	Y
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

**B**

A\BC	00	01	11	10
0	1	0	0	1
1	0	0	1	1

**C**

**A**

A\BC	00	01	11	10
0	0	1	1	0
1	0	1	1	0

**C**

**A**

# Karnaugh Maps: Visualization of algebra

		B			
A\BC		00	01	11	10
0	1	0	0	1	
1	0	0	1	1	

C

A

		B			
A\BC		00	01	11	10
0	0	1	1	0	
1	0	1	1	0	

C

A

●  $A'B'C' + A'BC' = A'C'$ ;  $ABC + ABC' = AB$

●  $A'B'C + A'BC + AB'C + ABC = A'C + AC = C$

Thus minimized function is

●  $X = A'C' + AB$      $Y = C$

# 4-variable Kmaps / Design

		<u>C</u>			
		00	01	11	10
A	00	1			1
	01		1		
	11				
	10	1			1
		<u>D</u>			
		B			

$$F(A,B,C,D) = ABC' + A' C' D + A' BC + ACD + ?$$

$$F(A,B,C,D) = B' D' + \underline{\hspace{2cm}}$$

		<u>C</u>			
		00	01	11	10
A	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	
		<u>D</u>			
		B			

Try them with Logisim

# 4-variable Kmaps / Design

		<u>C</u>			
		00	01	11	10
A	00	1			1
	01		1		
	11				
	10	1			1
		<u>D</u>			

$$F(A,B,C,D) = ABC' + A' C' D + A' BC + ACD \quad \text{+?}$$

$$F(A,B,C,D) = B' D' + A' BC' D$$

		<u>C</u>			
		00	01	11	10
A	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	
		<u>D</u>			

Try them with Logisim