 


# Final Exam Review


# Transistor: Digital Building Blocks

- Logically, each transistor acts as a switch
- Combined to implement logic functions (gates)
  - AND, OR, NOT
- Combined to build higher-level structures
  - Multiplexer, decoder, register, memory ...
  - Adder, multiplier ...
- Combined to build simple processor
  - LC-3


# Basic Logic Gates




*NOT*

 


*OR*

 

*NOR*

 

*AND*

 


*NAND*


# Propagation Delay

- Each gate has a propagation delay, typically fraction of a nanosecond ( $10^{-9}$  sec).
- Delays accumulate depending on the chain of gates the signals have to go through.
- Clock frequency of a processor is determined by the delay of the longest combinational path between storage elements, i.e. cycle time.


# Boolean Algebra

 


$$x \cdot 0 = 0$$

 


$$x \cdot 1 = x$$

 


$$x \cdot \bar{x} = 0$$

 

$$x + 0 = x$$

 

$$x + 1 = 1$$

 


$$x + \bar{x} = 1$$

Remember Identify, Domination,  
Negation Laws from Logic!
 
# DeMorgan's Law

- Converting AND to OR (with some help from NOT)
- Consider the following gate:




A	B	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as A OR B!

*To convert AND to OR  
(or vice versa),  
invert inputs and output.*

# Combinational Logic

## ● Cascading set of logic gates

 

What is the truth table?

# Truth Table (from circuit)

● Truth table for circuit on previous slide

A	B	C	W	X	Y	Z
0	0	0	0	0	0	1
0	0	1	0	1	1	1
0	1	0	0	1	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	0	0




# Decoder

●  $n$  inputs,  $2^n$  outputs


- exactly one output is 1 for each possible input pattern

*2-bit  
decoder*

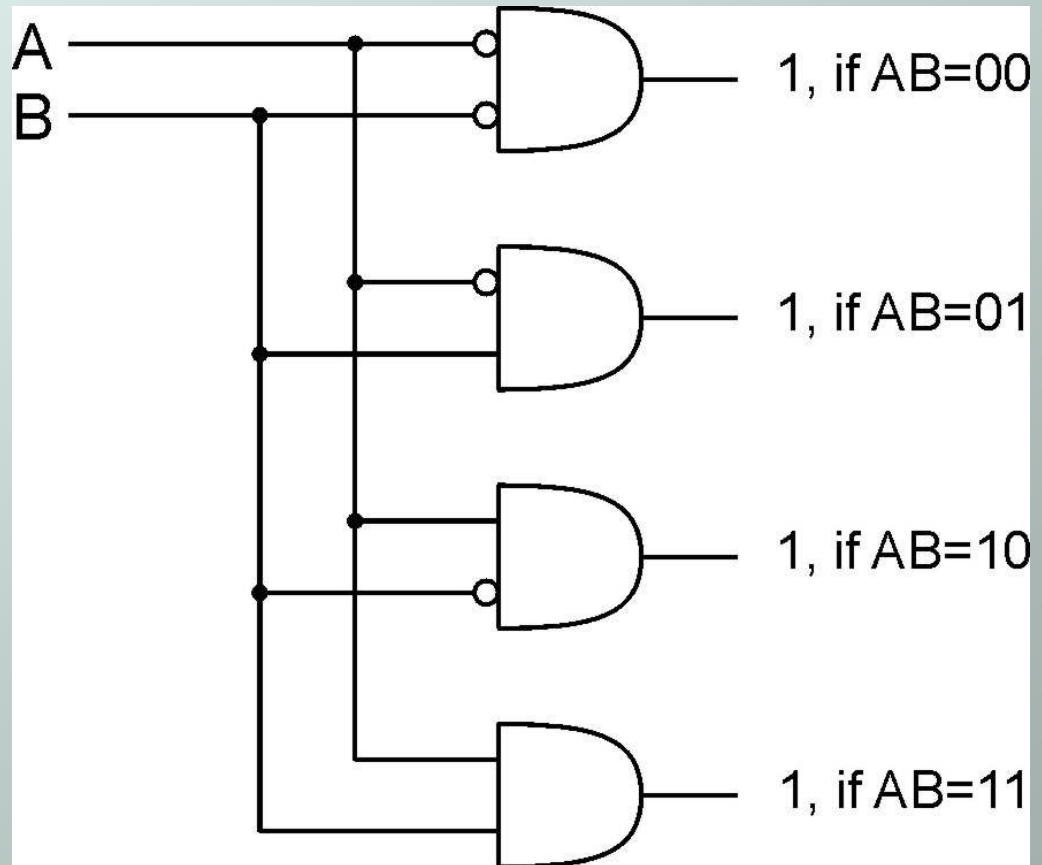

 
# Multiplexer (MUX)

- $n$ -bit selector and  $2^n$  inputs, one output
  - output equals one of the inputs, depending on selector



 
# Full Adder

- Add two bits and carry-in, produce one-bit sum and carry-out.




A	B	$C_{in}$	S	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Four-bit Adder



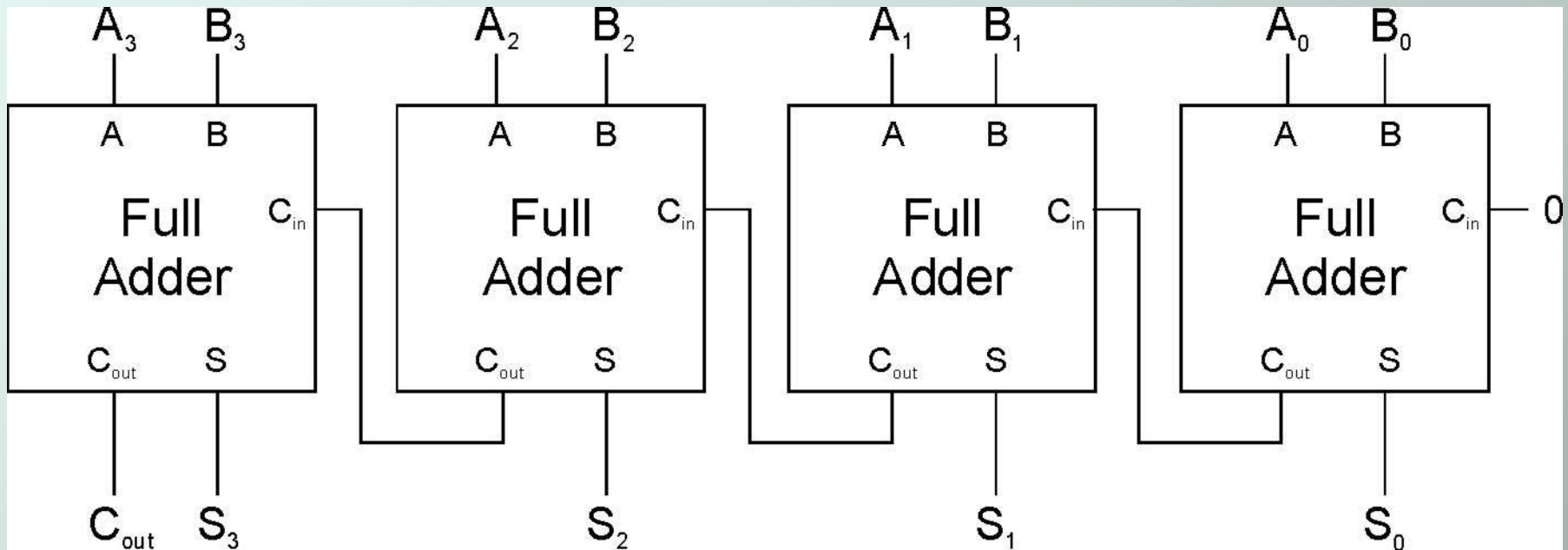

 
# Programmable Logic Array

- Front end reacts to specific inputs
- Back end defines the outputs
- Any truth table can be built
- Not necessarily minimal circuit!



Requires (at least) ten gates.

   

# Storage Elements & Sequential Circuits

# Combinational vs. Sequential

## ● Combinational Circuit



- always gives the same output for a given set of inputs
  - ex: adder always generates sum and carry, regardless of previous inputs

## ● Sequential Circuit

- stores information
- output depends on stored information (state) plus input
  - so a given input might produce different outputs, depending on the stored information
- *example*: ticket counter
  - advances when you push the button
  
# R-S Latch: Simple Storage Element

- R is used to “reset” or “clear” the element – set it to zero.
- S is used to “set” the element – set it to one.



- If both R and S are one, out could be either zero or one.
  - “quiescent” state -- holds its previous value
  - note: if a is 1, b is 0, and vice versa



# R-S Latch Summary

●  $R = S = 1$

- hold current value in latch

●  $S = 0, R=1$

- set value to 1

●  $R = 0, S = 1$


- set value to 0

●  $R = S = 0$


- both outputs equal one
- final state determined by electrical properties of gates
- *Don't do it!*
 
# Gated D-Latch

- Two inputs: D (data) and WE (write enable)
  - when **WE = 1**, latch is set to **value of D**
    - $S = \text{NOT}(D)$ ,  $R = D$
  - when **WE = 0**, latch holds **previous value**




# $2^2 \times 3$ Memory

 

# Finite State Machines

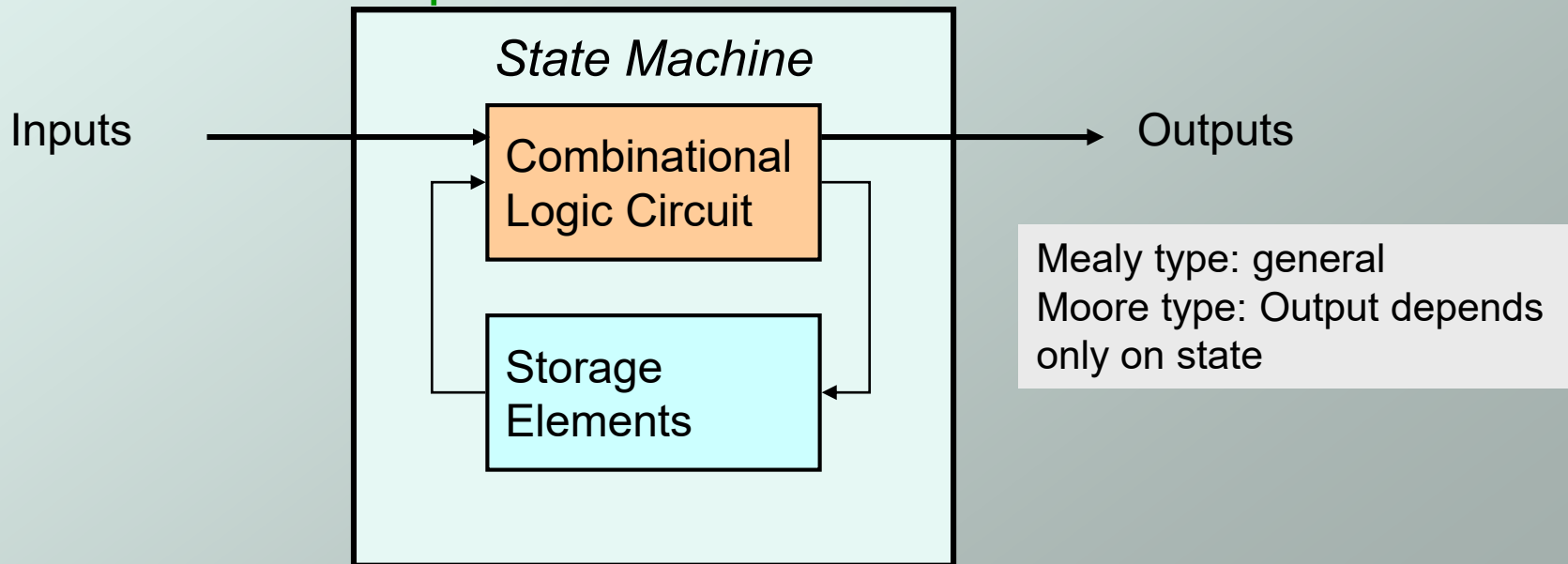
# State Machine

- A general sequential circuit
  - Combines combinational logic with storage
  - “Remembers” state, and changes output (and state) based on **inputs** and **current state**


 
# State Diagram

- Shows **states** and **actions** that cause a **transition** between states.




# Finite State Machine

- A description of a system with the following components:
  1. A finite number of **states**
  2. A finite number of external **inputs**
  3. A finite number of external **outputs**
  4. An explicit specification of all **state transitions**
  5. An explicit specification of what determines each external **output value**
  
- Often described by a state diagram.
  - Inputs trigger state transitions.
 
# The Clock

- Frequently, a **clock circuit** triggers transition from one state to the next.




- At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.



 
# Storage: Master-Slave Flipflop

- A pair of gated D-latches, to isolate *next* state from *current* state.




During 1<sup>st</sup> phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.

 During 2<sup>nd</sup> phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.





# Memory Hierarchy

# Review: Major Components of a Computer

 

# Review: Major Components of a Computer

 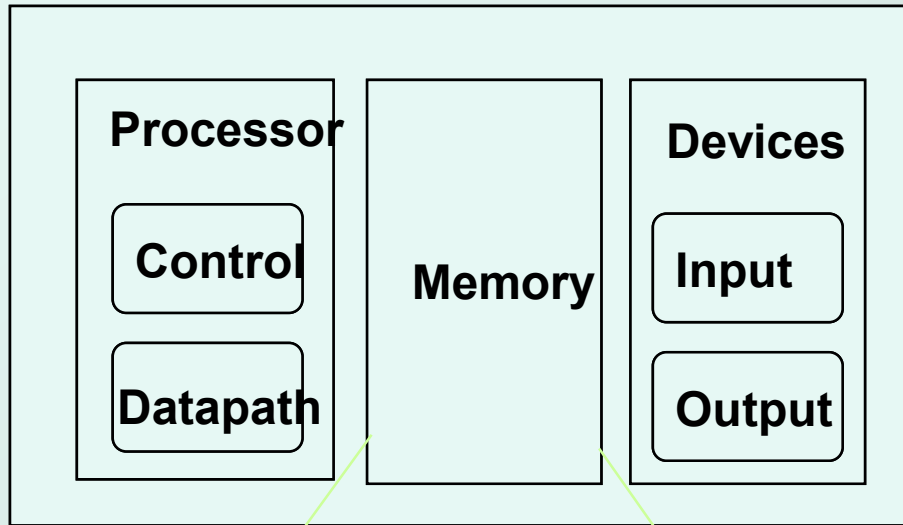


Level	Access time	Size	Cost/GB
Registers	0.25 ns	48+ 64,128, 32b	-
Cache L1,L2,L3	0.5 ns	5MB	125
Memory	1000 ns	8GB	4.0
SSD	100K ns		0.25
Disk	1000K ns	1 TB	0.02

# The Memory Hierarchy: Key facts and ideas (1)

- Programs keep getting bigger exponentially.
- Memory cost /bit
  - Faster technologies are expensive, slower are cheaper. Different by orders of magnitude
  - With time storage density goes up driving per bit cost down.
- Locality in program execution
  - Code/data used recently will likely be needed soon.
  - Code/data that is near the one recently used, will likely be needed soon.
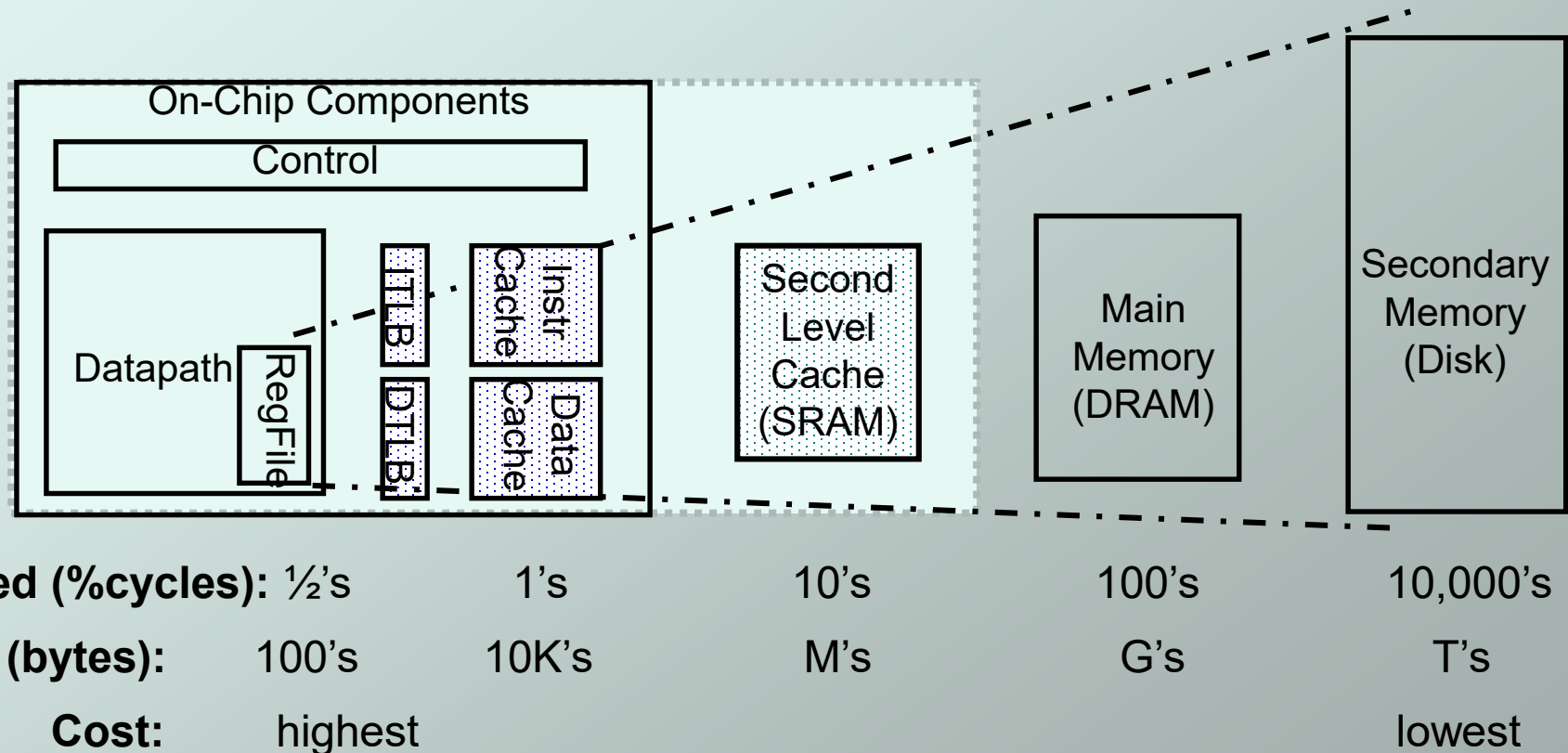
# A Typical Memory Hierarchy

- Take advantage of the **principle of locality** to present the user with as much memory as is available in the *cheapest* technology at the speed offered by the *fastest* technology



# Principle of Locality

- Programs access a small proportion of their address space at any time
- Temporal locality
  - Items accessed recently are likely to be accessed again soon
  - e.g., instructions in a loop, induction variables
- Spatial locality
  - Items near those accessed recently are likely to be accessed soon
  - E.g., sequential instruction access, array data

# Cache Misses

- On cache hit, CPU proceeds normally
- On cache miss
  - Stall the CPU pipeline
  - Fetch block from next level of hierarchy
  - Instruction cache miss
    - Restart instruction fetch
  - Data cache miss
    - Complete data access



# Multilevel Caches

- Primary cache attached to CPU
  - Small, but fast
- Level-2 cache services misses from primary cache
  - Larger, slower, but still faster than main memory
- Main memory services L-2 cache misses
- Some systems now include L-3 cache


# Virtual Memory

- Use main memory as a “cache” for secondary (disk) storage
  - Managed jointly by CPU hardware and the operating system (OS)
- Programs share main memory
  - Each gets a **private virtual address** space holding its frequently used code and data
  - Protected from other programs
- CPU and OS translate virtual addresses to physical addresses
  - VM “block” is called a page
  - VM translation “miss” is called a page fault


# Virtual vs. Physical Address

- Processor assumes a certain memory addressing scheme:
  - A block of data is called a virtual page
  - An address is called virtual (or logical) address
- Main memory may have a different addressing scheme:
  - Real memory address is called a physical address, MMU translates virtual address to physical address
  - Complete address translation table is large and must therefore reside in main memory
  - MMU contains TLB (translation lookaside buffer), which is a small cache of the address translation table

# Logical View of Segmentation

 


user space

 

physical memory space


# Segmentation Hardware

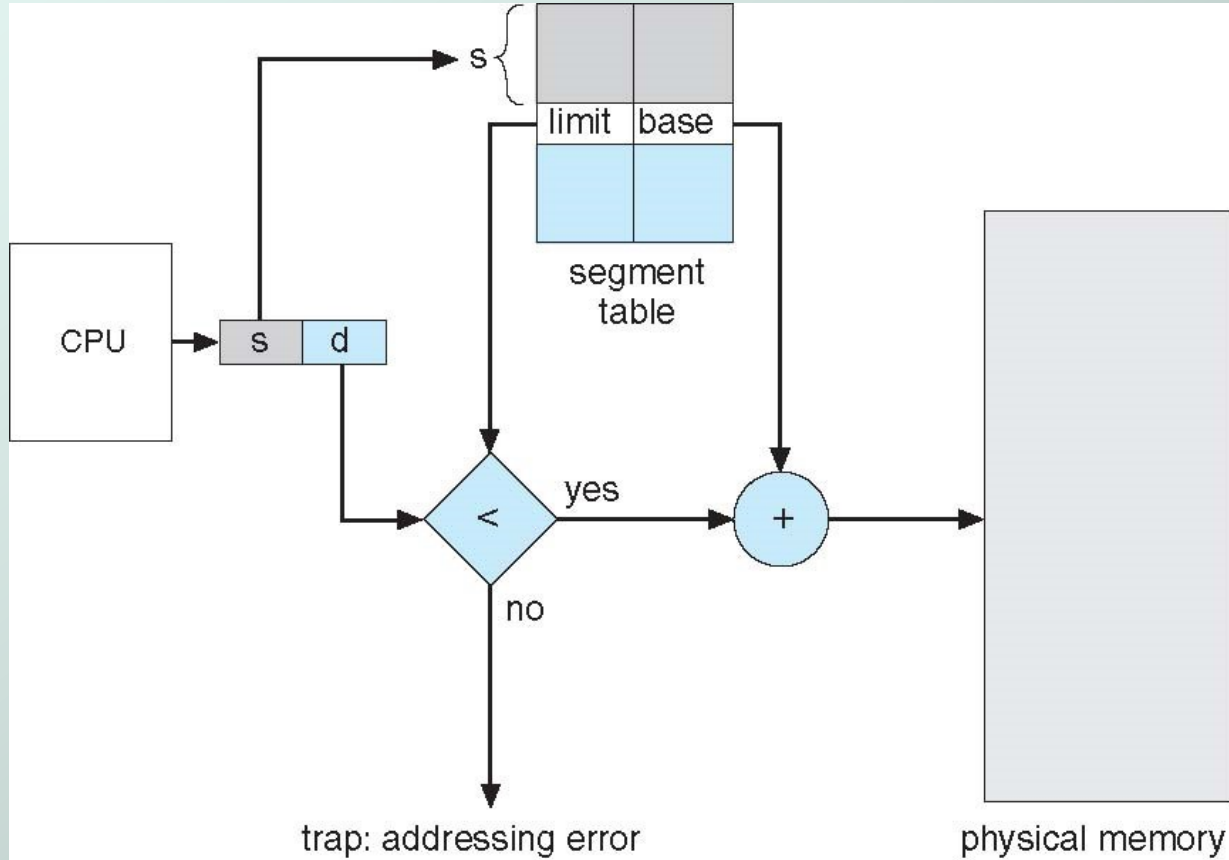

# Paging

- ❶ Physical address space of a process can be noncontiguous; process is allocated physical memory whenever the latter is available
  - Avoids external fragmentation
  - Avoids problem of varying sized memory chunks
- ❷ Divide physical memory into fixed-sized blocks called **frames**
  - Size is power of 2, between 512 bytes and 16 Mbytes
- ❸ Divide logical memory into blocks of same size called **pages**

# Paging Hardware

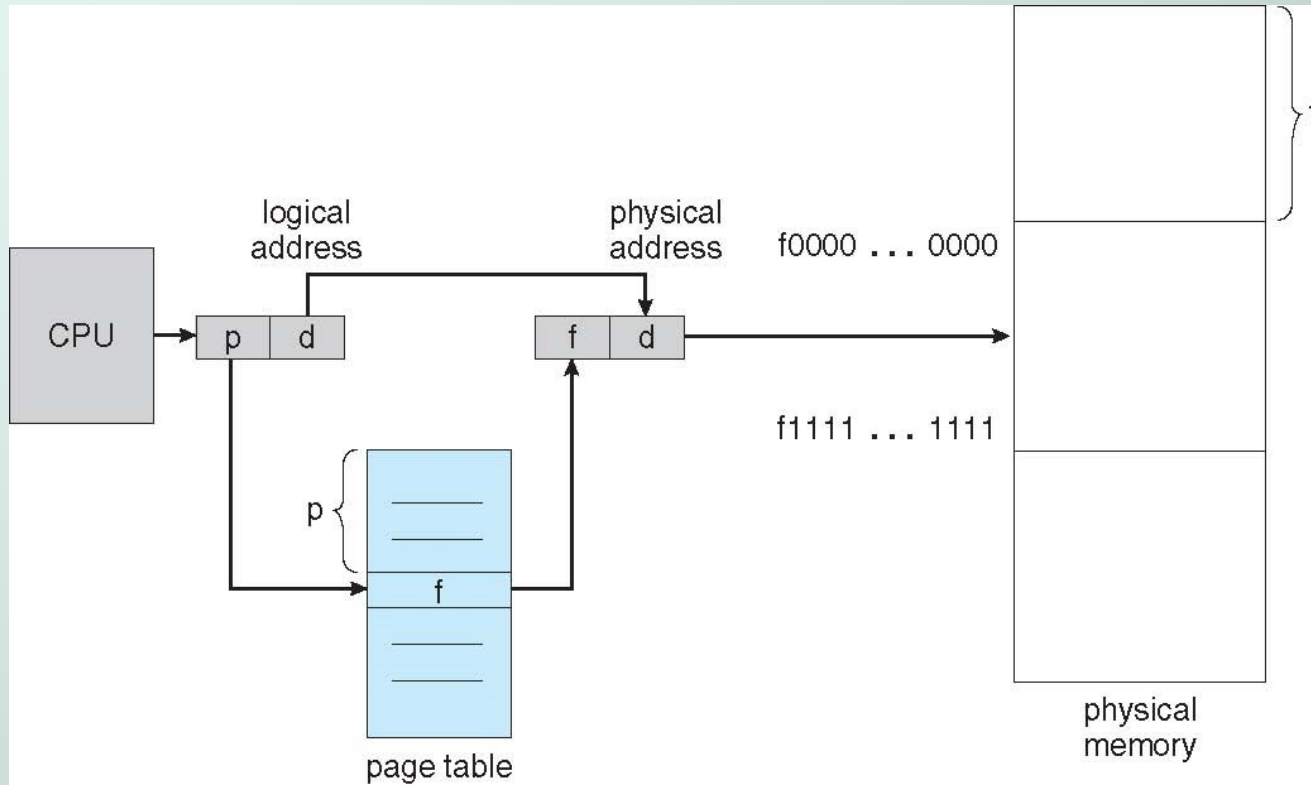

# Page Fault Penalty

- On page fault, the page must be fetched from disk
  - Takes millions of clock cycles
  - Handled by OS code
- Try to minimize page fault rate
  - Smart replacement algorithms



# 3-Level Cache Organization

	Intel Nehalem	AMD Opteron X4
L1 caches (per core)	<p>L1 I-cache: 32KB, 64-byte blocks, 4-way, approx LRU replacement, hit time n/a</p> <p>L1 D-cache: 32KB, 64-byte blocks, 8-way, approx LRU replacement, write-back/allocate, hit time n/a</p>	<p>L1 I-cache: 32KB, 64-byte blocks, 2-way, LRU replacement, hit time 3 cycles</p> <p>L1 D-cache: 32KB, 64-byte blocks, 2-way, LRU replacement, write-back/allocate, hit time 9 cycles</p>
L2 unified cache (per core)	256KB, 64-byte blocks, 8-way, approx LRU replacement, write-back/allocate, hit time n/a	512KB, 64-byte blocks, 16-way, approx LRU replacement, write-back/allocate, hit time n/a
L3 unified cache (shared)	8MB, 64-byte blocks, 16-way, replacement n/a, write-back/allocate, hit time n/a	2MB, 64-byte blocks, 32-way, replace block shared by fewest cores, write-back/allocate, hit time 32 cycles

n/a: data not available