 


Storage Elements & Sequential Circuits

LC-3 Data Path Revisited

Now Registers and
Memory



Combinational vs. Sequential

Combinational Circuit

- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs

Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
- *example:* ticket counter
 - advances when you push the button
 - output depends on previous state
- useful for building “memory” elements and “state machines”



Storage Elements

- **Static: use a circuit with feedback to save a bit of information**
 - flipflops
 - Static memories
- **Dynamic: Use charge at a node to represent a 1 or 0**
 - A cell in a dynamic memory
 - Fewer transistors hence cheaper
 - Need periodic refreshing, every few millisecs.
- **Both are volatile.**
- **Not considered here:**
 - ROM (read only memory): combinational
 - Flash memory: semiconductor, but work like disks

R-S Latch: Simple Storage Element

R is used to “reset” or “clear” the element – set it to zero.

  S is used to “set” the element – set it to one.




If both R and S are one, out could be either zero or one.


- “quiescent” state -- holds its previous value
- note: if a is 1, b is 0, and vice versa

Clearing the R-S latch

 Suppose we start with output = 1, then change R to zero.




Output changes to zero.

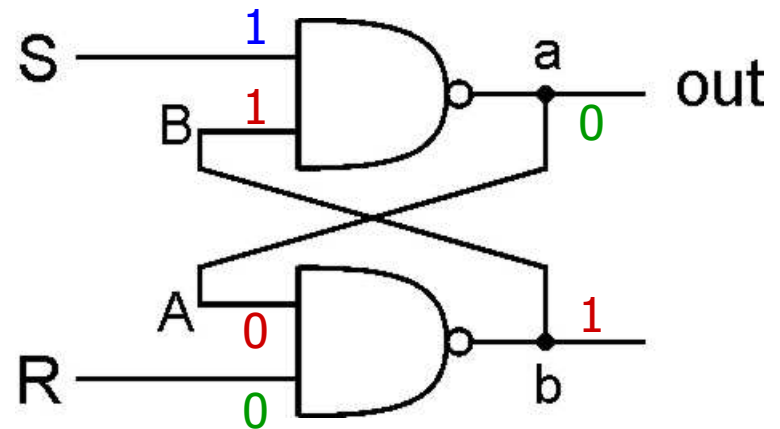


Then set R=1 to “store” value in quiescent state.

Setting the R-S Latch

 Suppose we start with output = 0, then change S to zero.



Output changes to one.

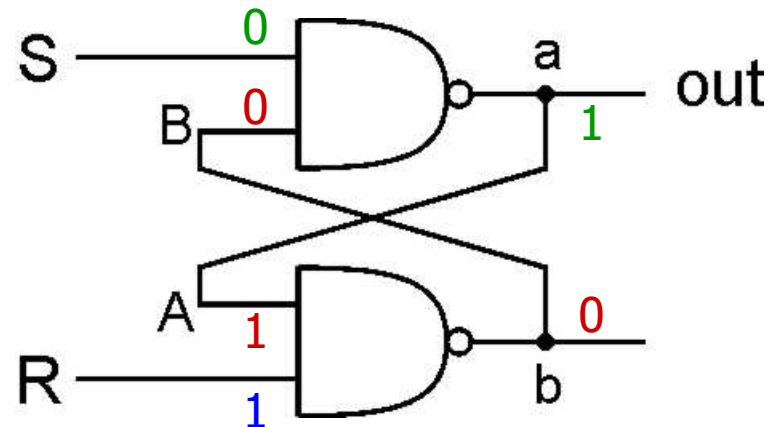

Then set S=1 to “store” value in quiescent state.

R-S Latch Summary

$R = S = 1$

- **hold current value in latch**

$S = 0, R=1$

- **set value to 1**

$R = 0, S = 1$

- **set value to 0**


$R = S = 0$

- **both outputs equal one**
- **final state determined by electrical properties of gates**
- *Don't do it!*

Gated D-Latch

Two inputs: D (data) and WE (write enable)

 
- when **WE = 1**, latch is set to **value of D**
 - $S = \text{NOT}(D)$, $R = D$
- when **WE = 0**, latch holds **previous value**
 - $S = R = 1$



Register


A register stores a multi-bit value.

 - We use a collection of D-latches, all controlled by a common WE.
- When WE=1, n-bit value D is written to register.




Flip-flops

 D Flip-flop: a storage element, can be edge-triggered (available in logisim)



Rising edge: input sampled

 

D	Next Q
0	0
1	1



State Q is always available

Registers

A register is a row of storage element.

Register with parallel load with a Load control line

Clock is often implied

  


Representing Multi-bit Values

Number bits from right (0) to left (n-1)

- just a convention -- could be left to right, but must be consistent

Use brackets to denote range:

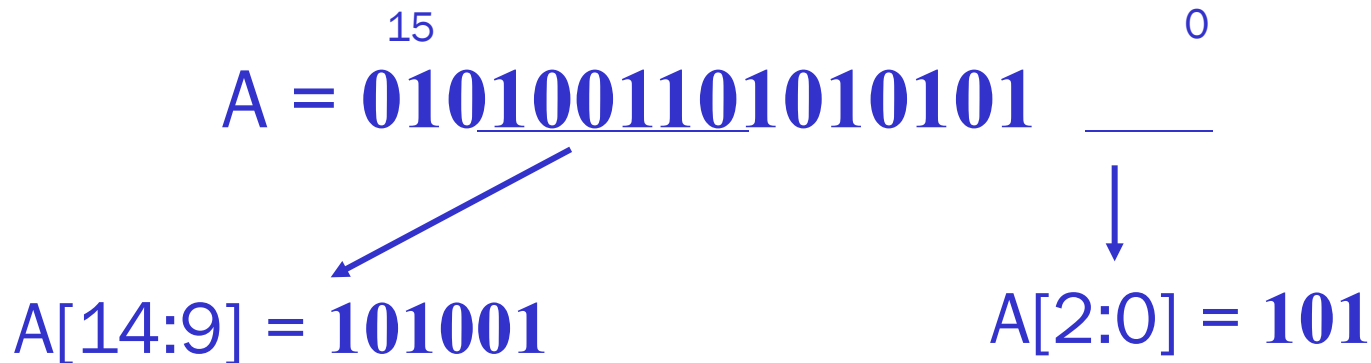$D[l:r]$ denotes bit l to bit r , from *left to right*




May also see $A\langle 14:9 \rangle$,
especially in hardware block diagrams.

Memory

Now that we know how to store bits, we can build a memory – a logical $k \times m$ array of stored bits.

Address Space:
number of locations
(usually a power of 2)


$k = 2^n$
locations

 

Addressability:
number of bits per location
(e.g., byte-addressable)

m bits

2² x 3 Memory

 

More Memory Details

This is a not the way actual memory is implemented.

- fewer transistors, much more dense, relies on electrical properties

But the logical structure is very similar.

- address decoder
- word select line
- word write enable

Two basic kinds of **RAM** (Random Access Memory)

Static RAM (SRAM)

- fast, maintains data as long as power applied

Dynamic RAM (DRAM)

- slower but denser, bit storage decays – must be periodically refreshed


Also, non-volatile memories: ROM, PROM, flash, ...

Finite State Machines

State Machine



A general sequential circuit

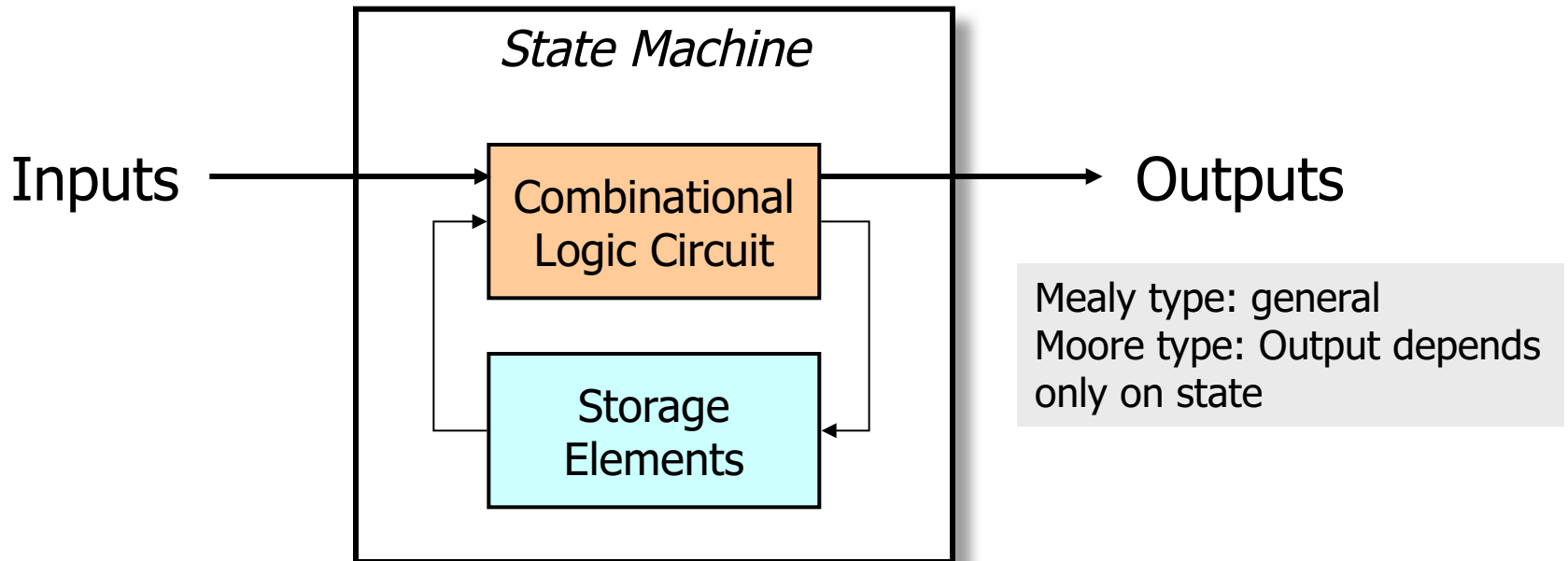- Combines combinational logic with storage
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**



Combinational vs. Sequential

Two types of “combination” locks

  

Combinational

Success depends only on the **values**, not the order in which they are set.

Sequential

Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).

State

The **state** of a system is a **snapshot** of **all the relevant elements** of the system at the moment the snapshot is taken.

Examples:

- The state of a basketball game can be represented by the scoreboard.
 - Number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X' s and O' s on the board.


State of Sequential Lock

Our lock example has four different states, labelled A-D:


- A:** The lock is **not open**,
and no relevant operations have been performed.
- B:** The lock is **not open**,
and the user has completed the **R-13** operation.
- C:** The lock is **not open**,
and the user has completed **R-13**, followed by **L-22**.
- D:** The lock is **open**.

State Diagram

 Shows **states** and **actions** that cause a **transition** between states.



State Table for the lock

 

Input	Present State	Next State	Output/action
R-32	A	B	-
Not R-32	A	A	-
L-22	B	C	-
Not L-22	B	A	-
R-3	C	D	-
Not R-3	C	A	-
R-13	D	B	Open
Not R-13	D	A	Open

Finite State Machine

A description of a system with the following components:


1. A finite number of **states**
2. A finite number of external **inputs**
3. A finite number of external **outputs**
4. An explicit specification of all **state transitions**
5. An explicit specification of what determines each external **output value**

Often described by a state diagram.

- Inputs trigger state transitions.
- Outputs are associated with each state (or with each transition).

The Clock

 Frequently, a **clock circuit** triggers transition from one state to the next.



At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.

- Not always required. In lock example, the input itself triggers a transition.


Implementing a Finite State Machine

Combinational logic

- Determine outputs and next state.

Storage elements


- Maintain state representation.

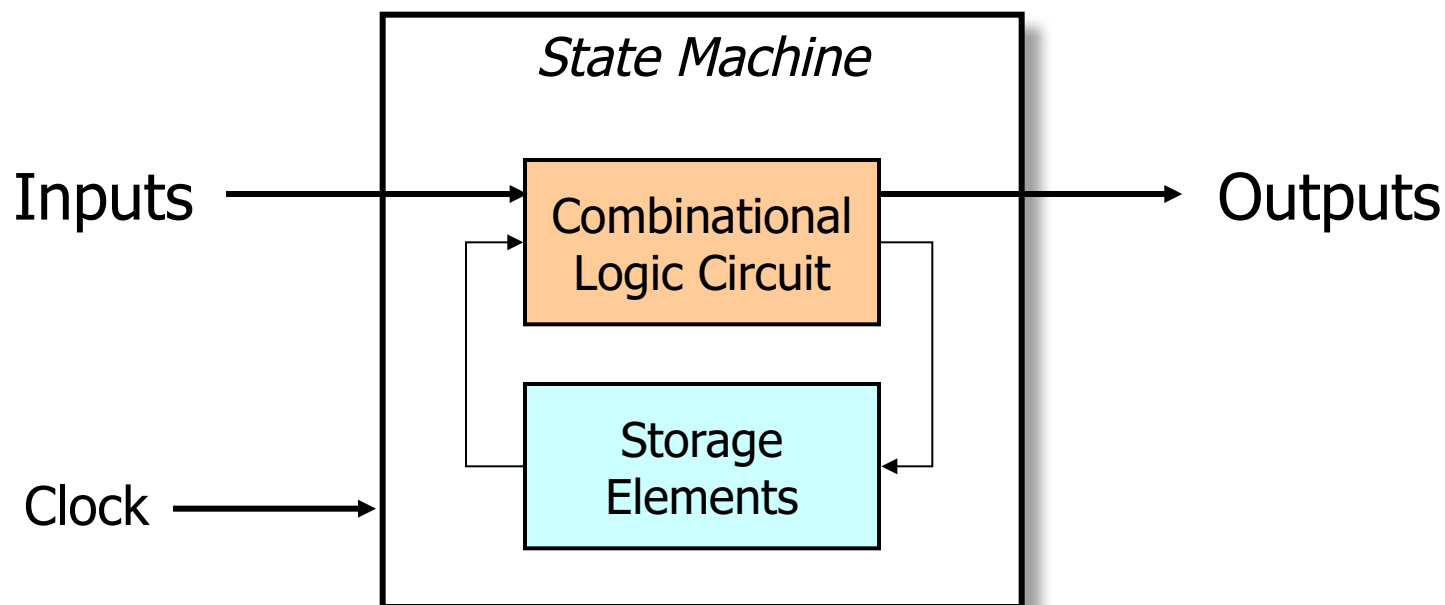

Storage: Master-Slave Flipflop

Skip: there are several Possible designs

 A pair of gated D-latches, to isolate *next* state from *current* state.




During 1st phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.

During 2nd phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.

Analyzing a FSM: Logic Circuit to State Diagram

- 1. Describe combinational circuit outputs using Boolean algebra.**
- 2. Get the State Table for all possible Input/state combinations.**
 - 1. Causes: Input, Present State**
 - 2. Effects: Next State, Outputs (if different from State)**
- 3. Get a state diagram. It provides a graphical description of the behavior.**

Example 1: Analyze this FSM

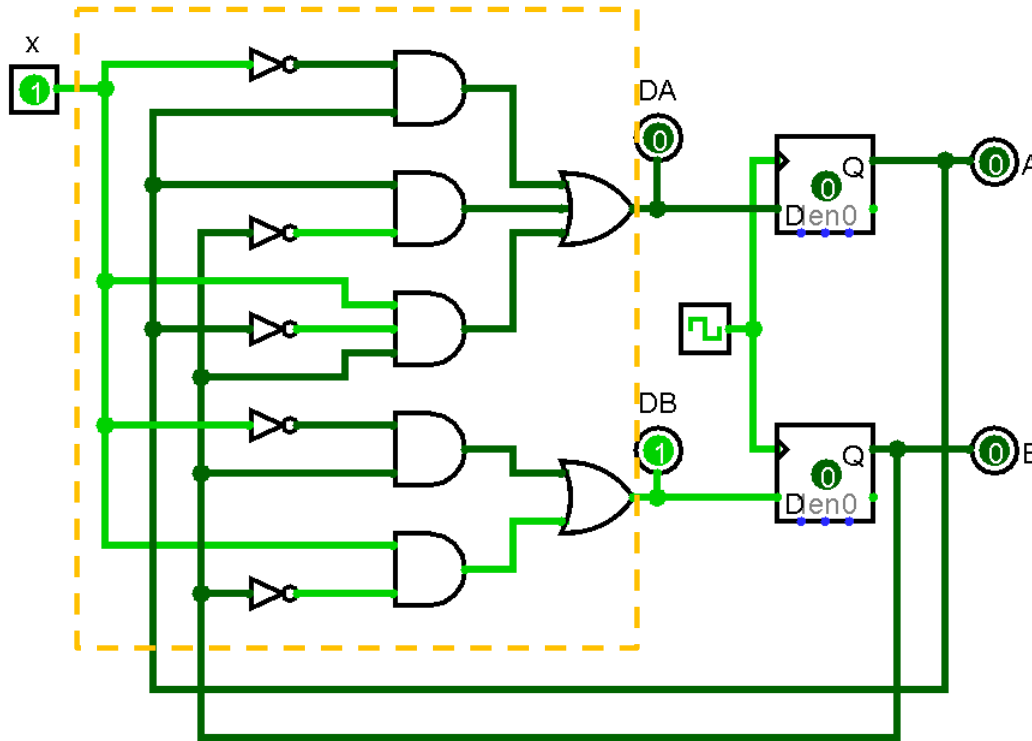

Input: x
 State: A, B
 Output: A, B

Combinational block
 In: x, A, B Out: DA, DB

$$DA = \overline{x}A + A\overline{B} + x\overline{A}B$$

$$DB = \overline{x}B + x\overline{B}$$

Example 1: Analyze this FSM (cont)

$$DA = \bar{x}A + A\bar{B} + x\bar{A}\bar{B}$$

$$DB = \bar{x}B + x\bar{B}$$


Input	Present State		Next State	
	A	B	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Example 1: Analyze this FSM (last)

State Diagram

State Table

Input X	Present State		Next State	
	A	B	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

 

It is an up counter

Designing a FSM: Specification to Circuit

Reverse of Analysis we have seen.


1. **Obtain a State Diagram using the specification. This is the challenging part. Determine the number of flip-flops needed (We will only use D type for convenience) and assign each state a unique binary combination.**
2. **Get the State Table for all possible Input/state combinations.**
 1. **Causes: Input, Present State**
 2. **Effects: Next State, Outputs (if different from State)**
3. **The Combinational circuit truth table is given by the State Table itself (Next state values are the D inputs). Design the combinational circuit. Optimize it as needed.**
4. **Get complete circuit with Combinational Logic, flip-flops attached.**
5. **Simulate and verify the design.**

Example 2: Danger Sign design from P&P


A blinking traffic sign

- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as **switch** is turned on)

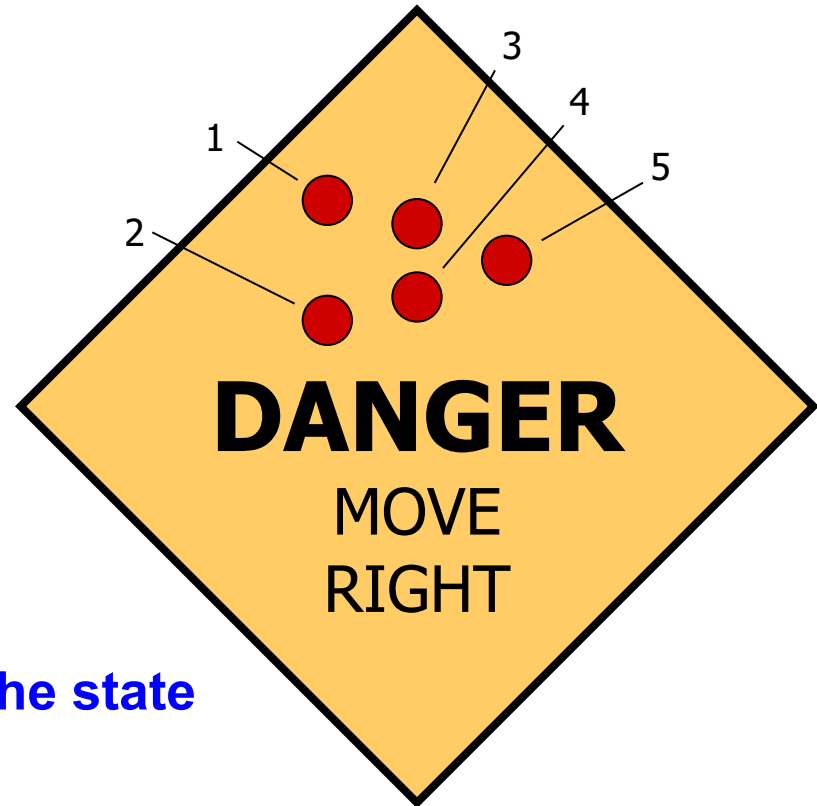- **Input: Switch**
- **Outputs: Z, Y, X**
- **States: 4 (bits S1, S0)**
- **Choose: output depends on the state**



Traffic Sign State Diagram

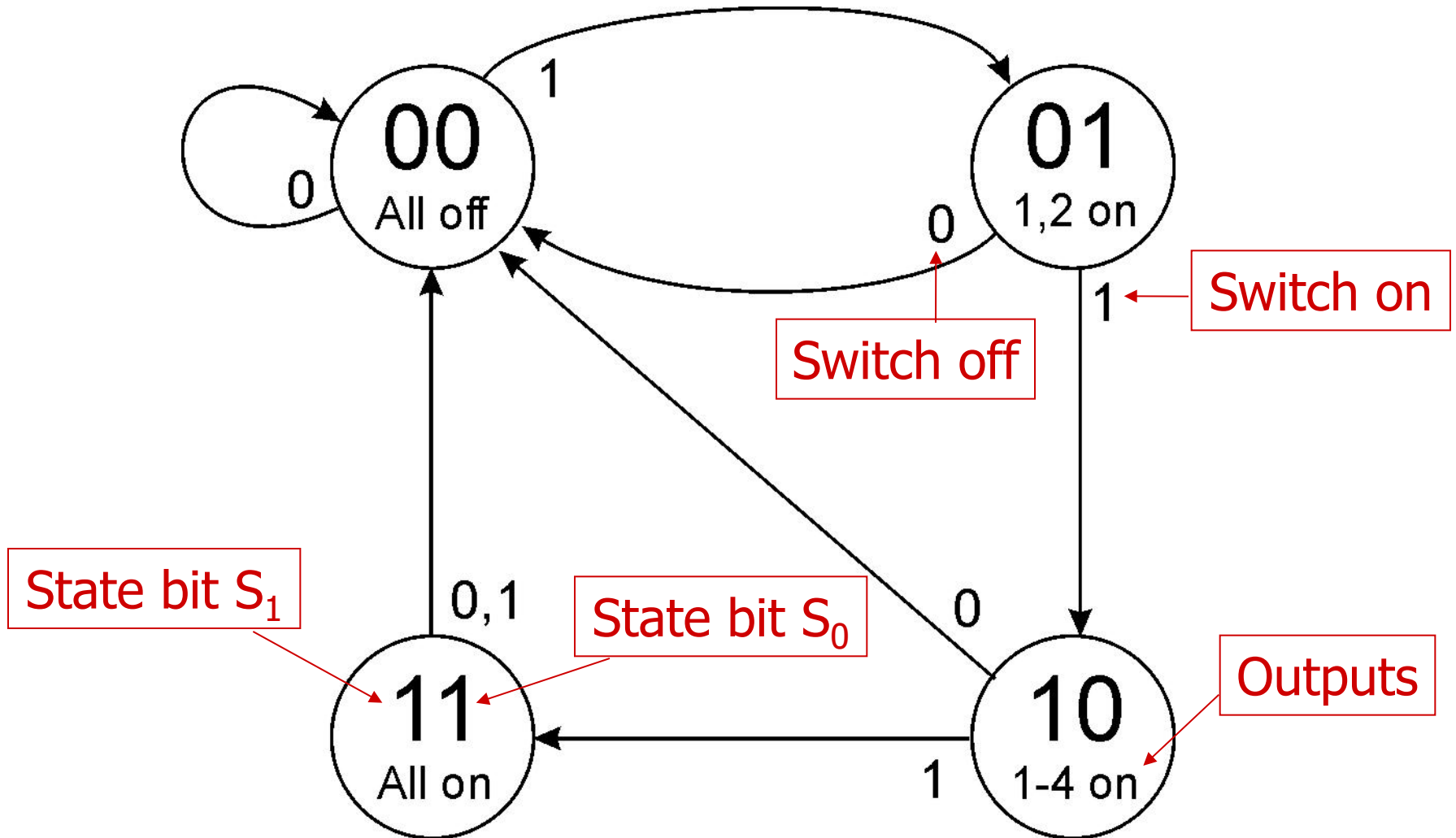

Transition on each clock cycle.

State Table

Input	Present State		Next State		Output
In	S1	S0	S1	S0	ZYX
0	0	0	0	0	000
0	0	1	0	0	100
0	1	0	0	0	110
0	1	1	0	0	111
1	0	0	0	1	000
1	0	1	1	0	100
1	1	0	1	1	110
1	1	1	0	0	111

See Logisim implementation
Present state: flipflop output
Next state: flipflop D inputs

Traffic Sign Truth Tables (from book)

Outputs

(depend only on state: S_1S_0)

S_1	S_0	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1


Next State: $S_1' S_0'$

(depend on state and input)

In	S_1	S_0	S_1'	S_0'
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Whenever $In=0$, next state is 00.

Traffic Sign Logic (from book)

 

This design is not optimized. Try Logisim to optimize.

Any edge triggered flip-flop will work.

Master-slave flipflop

From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-3 as an example.

Combinational Logic

- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements